

THE ART OF ELECTRONICS

Third Edition

Paul Horowitz HARVARD UNIVERSITY

Winfield Hill ROWLAND INSTITUTE AT HARVARD



CAMBRIDGE
UNIVERSITY PRESS

CAMBRIDGE
UNIVERSITY PRESS

32 Avenue of the Americas, New York, NY 10013-2473, USA

Cambridge University Press is part of the University of Cambridge.

It furthers the University's mission by disseminating knowledge in the pursuit of education, learning, and research at the highest international levels of excellence.

www.cambridge.org

Information on this title: www.cambridge.org/9780521809269

© Cambridge University Press, 1980, 1989, 2015

This publication is in copyright. Subject to statutory exception and to the provisions of relevant collective licensing agreements, no reproduction of any part may take place without the written permission of Cambridge University Press.

First published 1980

Second edition 1989

Third edition 2015

Printed in the United States of America

A catalog record for this publication is available from the British Library.

ISBN 978-0-521-80926-9 Hardback

Cambridge University Press has no responsibility for the persistence or accuracy of URLs for external or third-party Internet websites referred to in this publication and does not guarantee that any content on such websites is, or will remain, accurate or appropriate.

CONTENTS

List of Tables	xxii		
Preface to the First Edition	xxv		
Preface to the Second Edition	xxvii		
Preface to the Third Edition	xxix		
ONE: Foundations	1		
1.1 Introduction	1		
1.2 Voltage, current, and resistance	1		
1.2.1 Voltage and current	1		
1.2.2 Relationship between voltage and current: resistors	3		
1.2.3 Voltage dividers	7		
1.2.4 Voltage sources and current sources	8		
1.2.5 Thévenin equivalent circuit	9		
1.2.6 Small-signal resistance	12		
1.2.7 An example: “It’s too hot!”	13		
1.3 Signals	13		
1.3.1 Sinusoidal signals	14		
1.3.2 Signal amplitudes and decibels	14		
1.3.3 Other signals	15		
1.3.4 Logic levels	17		
1.3.5 Signal sources	17		
1.4 Capacitors and ac circuits	18		
1.4.1 Capacitors	18		
1.4.2 <i>RC</i> circuits: <i>V</i> and <i>I</i> versus time	21		
1.4.3 Differentiators	25		
1.4.4 Integrators	26		
1.4.5 Not quite perfect. . .	28		
1.5 Inductors and transformers	28		
1.5.1 Inductors	28		
1.5.2 Transformers	30		
1.6 Diodes and diode circuits	31		
1.6.1 Diodes	31		
1.6.2 Rectification	31		
1.6.3 Power-supply filtering	32		
1.6.4 Rectifier configurations for power supplies	33		
		1.6.5 Regulators	34
		1.6.6 Circuit applications of diodes	35
		1.6.7 Inductive loads and diode protection	38
		1.6.8 Interlude: inductors as friends	39
		1.7 Impedance and reactance	40
		1.7.1 Frequency analysis of reactive circuits	41
		1.7.2 Reactance of inductors	44
		1.7.3 Voltages and currents as complex numbers	44
		1.7.4 Reactance of capacitors and inductors	45
		1.7.5 Ohm’s law generalized	46
		1.7.6 Power in reactive circuits	47
		1.7.7 Voltage dividers generalized	48
		1.7.8 <i>RC</i> highpass filters	48
		1.7.9 <i>RC</i> lowpass filters	50
		1.7.10 <i>RC</i> differentiators and integrators in the frequency domain	51
		1.7.11 Inductors versus capacitors	51
		1.7.12 Phasor diagrams	51
		1.7.13 “Poles” and decibels per octave	52
		1.7.14 Resonant circuits	52
		1.7.15 <i>LC</i> filters	54
		1.7.16 Other capacitor applications	54
		1.7.17 Thévenin’s theorem generalized	55
		1.8 Putting it all together – an AM radio	55
		1.9 Other passive components	56
		1.9.1 Electromechanical devices: switches	56
		1.9.2 Electromechanical devices: relays	59
		1.9.3 Connectors	59
		1.9.4 Indicators	61
		1.9.5 Variable components	63
		1.10 A parting shot: confusing markings and itty-bitty components	64
		1.10.1 Surface-mount technology: the joy and the pain	65

Additional Exercises for Chapter 1	66	2.6.1	Regulated power supply	123
Review of Chapter 1	68	2.6.2	Temperature controller	123
		2.6.3	Simple logic with transistors and diodes	123
TWO: Bipolar Transistors	71		Additional Exercises for Chapter 2	124
2.1 Introduction	71		Review of Chapter 2	126
2.1.1 First transistor model: current amplifier	72	THREE: Field-Effect Transistors	131	
2.2 Some basic transistor circuits	73	3.1 Introduction	131	
2.2.1 Transistor switch	73	3.1.1 FET characteristics	131	
2.2.2 Switching circuit examples	75	3.1.2 FET types	134	
2.2.3 Emitter follower	79	3.1.3 Universal FET characteristics	136	
2.2.4 Emitter followers as voltage regulators	82	3.1.4 FET drain characteristics	137	
2.2.5 Emitter follower biasing	83	3.1.5 Manufacturing spread of FET characteristics	138	
2.2.6 Current source	85	3.1.6 Basic FET circuits	140	
2.2.7 Common-emitter amplifier	87	3.2 FET linear circuits	141	
2.2.8 Unity-gain phase splitter	88	3.2.1 Some representative JFETs: a brief tour	141	
2.2.9 Transconductance	89	3.2.2 JFET current sources	142	
2.3 Ebers–Moll model applied to basic tran- sistor circuits	90	3.2.3 FET amplifiers	146	
2.3.1 Improved transistor model: transconductance amplifier	90	3.2.4 Differential amplifiers	152	
2.3.2 Consequences of the Ebers–Moll model: rules of thumb for transistor design	91	3.2.5 Oscillators	155	
2.3.3 The emitter follower revisited	93	3.2.6 Source followers	156	
2.3.4 The common-emitter amplifier revisited	93	3.2.7 FETs as variable resistors	161	
2.3.5 Biasing the common-emitter amplifier	96	3.2.8 FET gate current	163	
2.3.6 An aside: the perfect transistor	99	3.3 A closer look at JFETs	165	
2.3.7 Current mirrors	101	3.3.1 Drain current versus gate voltage	165	
2.3.8 Differential amplifiers	102	3.3.2 Drain current versus drain-source voltage: output conductance	166	
2.4 Some amplifier building blocks	105	3.3.3 Transconductance versus drain current	168	
2.4.1 Push–pull output stages	106	3.3.4 Transconductance versus drain voltage	170	
2.4.2 Darlington connection	109	3.3.5 JFET capacitance	170	
2.4.3 Bootstrapping	111	3.3.6 Why JFET (versus MOSFET) amplifiers?	170	
2.4.4 Current sharing in paralleled BJTs	112	3.4 FET switches	171	
2.4.5 Capacitance and Miller effect	113	3.4.1 FET analog switches	171	
2.4.6 Field-effect transistors	115	3.4.2 Limitations of FET switches	174	
2.5 Negative feedback	115	3.4.3 Some FET analog switch examples	182	
2.5.1 Introduction to feedback	116	3.4.4 MOSFET logic switches	184	
2.5.2 Gain equation	116	3.5 Power MOSFETs	187	
2.5.3 Effects of feedback on amplifier circuits	117	3.5.1 High impedance, thermal stability	187	
2.5.4 Two important details	120	3.5.2 Power MOSFET switching parameters	192	
2.5.5 Two examples of transistor amplifiers with feedback	121			
2.6 Some typical transistor circuits	123			

3.5.3	Power switching from logic levels	192	4.5	A detailed look at selected op-amp circuits	254
3.5.4	Power switching cautions	196	4.5.1	Active peak detector	254
3.5.5	MOSFETs versus BJTs as high-current switches	201	4.5.2	Sample-and-hold	256
3.5.6	Some power MOSFET circuit examples	202	4.5.3	Active clamp	257
3.5.7	IGBTs and other power semiconductors	207	4.5.4	Absolute-value circuit	257
3.6	MOSFETs in linear applications	208	4.5.5	A closer look at the integrator	257
3.6.1	High-voltage piezo amplifier	208	4.5.6	A circuit cure for FET leakage	259
3.6.2	Some depletion-mode circuits	209	4.5.7	Differentiators	260
3.6.3	Paralleling MOSFETs	212	4.6	Op-amp operation with a single power supply	261
3.6.4	Thermal runaway	214	4.6.1	Biasing single-supply ac amplifiers	261
Review of Chapter 3		219	4.6.2	Capacitive loads	264
FOUR: Operational Amplifiers		223	4.6.3	“Single-supply” op-amps	265
4.1	Introduction to op-amps – the “perfect component”	223	4.6.4	Example: voltage-controlled oscillator	267
4.1.1	Feedback and op-amps	223	4.6.5	VCO implementation: through-hole versus surface-mount	268
4.1.2	Operational amplifiers	224	4.6.6	Zero-crossing detector	269
4.1.3	The golden rules	225	4.6.7	An op-amp table	270
4.2	Basic op-amp circuits	225	4.7	Other amplifiers and op-amp types	270
4.2.1	Inverting amplifier	225	4.8	Some typical op-amp circuits	274
4.2.2	Noninverting amplifier	226	4.8.1	General-purpose lab amplifier	274
4.2.3	Follower	227	4.8.2	Stuck-node tracer	276
4.2.4	Difference amplifier	227	4.8.3	Load-current-sensing circuit	277
4.2.5	Current sources	228	4.8.4	Integrating suntan monitor	278
4.2.6	Integrators	230	4.9	Feedback amplifier frequency compensation	280
4.2.7	Basic cautions for op-amp circuits	231	4.9.1	Gain and phase shift versus frequency	281
4.3	An op-amp smorgasbord	232	4.9.2	Amplifier compensation methods	282
4.3.1	Linear circuits	232	4.9.3	Frequency response of the feedback network	284
4.3.2	Nonlinear circuits	236	Additional Exercises for Chapter 4		287
4.3.3	Op-amp application: triangle-wave oscillator	239	Review of Chapter 4		288
4.3.4	Op-amp application: pinch-off voltage tester	240	FIVE: Precision Circuits		292
4.3.5	Programmable pulse-width generator	241	5.1	Precision op-amp design techniques	292
4.3.6	Active lowpass filter	241	5.1.1	Precision versus dynamic range	292
4.4	A detailed look at op-amp behavior	242	5.1.2	Error budget	293
4.4.1	Departure from ideal op-amp performance	243	5.2	An example: the millivoltmeter, revisited	293
4.4.2	Effects of op-amp limitations on circuit behavior	249	5.2.1	The challenge: 10 mV, 1%, 10 M Ω , 1.8 V single supply	293
4.4.3	Example: sensitive millivoltmeter	253	5.2.2	The solution: precision RRIO current source	294
4.4.4	Bandwidth and the op-amp current source	254	5.3	The lessons: error budget, unspecified parameters	295

5.4	Another example: precision amplifier with null offset	297	5.11.3	Selecting an auto-zero op-amp	338
5.4.1	Circuit description	297	5.11.4	Auto-zero miscellany	340
5.5	A precision-design error budget	298	5.12	Designs by the masters: Agilent's accurate DMMs	342
5.5.1	Error budget	299	5.12.1	It's <i>impossible!</i>	342
5.6	Component errors	299	5.12.2	Wrong – it <i>is</i> possible!	342
5.6.1	Gain-setting resistors	300	5.12.3	Block diagram: a simple plan	343
5.6.2	The holding capacitor	300	5.12.4	The 34401A 6.5-digit front end	343
5.6.3	Nulling switch	300	5.12.5	The 34420A 7.5-digit frontend	344
5.7	Amplifier input errors	301	5.13	Difference, differential, and instrumentation amplifiers: introduction	347
5.7.1	Input impedance	302	5.14	Difference amplifier	348
5.7.2	Input bias current	302	5.14.1	Basic circuit operation	348
5.7.3	Voltage offset	304	5.14.2	Some applications	349
5.7.4	Common-mode rejection	305	5.14.3	Performance parameters	352
5.7.5	Power-supply rejection	306	5.14.4	Circuit variations	355
5.7.6	Nulling amplifier: input errors	306	5.15	Instrumentation amplifier	356
5.8	Amplifier output errors	307	5.15.1	A first (but naive) guess	357
5.8.1	Slew rate: general considerations	307	5.15.2	Classic three-op-amp instrumentation amplifier	357
5.8.2	Bandwidth and settling time	308	5.15.3	Input-stage considerations	358
5.8.3	Crossover distortion and output impedance	309	5.15.4	A “roll-your-own” instrumentation amplifier	359
5.8.4	Unity-gain power buffers	311	5.15.5	A riff on robust input protection	362
5.8.5	Gain error	312	5.16	Instrumentation amplifier miscellany	362
5.8.6	Gain nonlinearity	312	5.16.1	Input current and noise	362
5.8.7	Phase error and “active compensation”	314	5.16.2	Common-mode rejection	364
5.9	RRIO op-amps: the good, the bad, and the ugly	315	5.16.3	Source impedance and CMRR	365
5.9.1	Input issues	316	5.16.4	EMI and input protection	365
5.9.2	Output issues	316	5.16.5	Offset and CMRR trimming	366
5.10	Choosing a precision op-amp	319	5.16.6	Sensing at the load	366
5.10.1	“Seven precision op-amps”	319	5.16.7	Input bias path	366
5.10.2	Number per package	322	5.16.8	Output voltage range	366
5.10.3	Supply voltage, signal range	322	5.16.9	Application example: current source	367
5.10.4	Single-supply operation	322	5.16.10	Other configurations	368
5.10.5	Offset voltage	323	5.16.11	Chopper and auto-zero instrumentation amplifiers	370
5.10.6	Voltage noise	323	5.16.12	Programmable gain instrumentation amplifiers	370
5.10.7	Bias current	325	5.16.13	Generating a differential output	372
5.10.8	Current noise	326	5.17	Fully differential amplifiers	373
5.10.9	CMRR and PSRR	328	5.17.1	Differential amplifiers: basic concepts	374
5.10.10	GBW, f_T , slew rate and “ m ,” and settling time	328	5.17.2	Differential amplifier application example: wideband analog link	380
5.10.11	Distortion	329	5.17.3	Differential-input ADCs	380
5.10.12	“Two out of three isn't bad”: creating a perfect op-amp	332	5.17.4	Impedance matching	382
5.11	Auto-zeroing (chopper-stabilized) amplifiers	333			
5.11.1	Auto-zero op-amp properties	334			
5.11.2	When to use auto-zero op-amps	338			

5.17.5	Differential amplifier selection criteria	383	7.2.4	Timing with digital counters	465
	Review of Chapter 5	388		Review of Chapter 7	470
SIX: Filters		391	EIGHT: Low-Noise Techniques		473
6.1	Introduction	391	8.1	“Noise”	473
6.2	Passive filters	391	8.1.1	Johnson (Nyquist) noise	474
6.2.1	Frequency response with <i>RC</i> filters	391	8.1.2	Shot noise	475
6.2.2	Ideal performance with <i>LC</i> filters	393	8.1.3	$1/f$ noise (flicker noise)	476
6.2.3	Several simple examples	393	8.1.4	Burst noise	477
6.2.4	Enter active filters: an overview	396	8.1.5	Band-limited noise	477
6.2.5	Key filter performance criteria	399	8.1.6	Interference	478
6.2.6	Filter types	400	8.2	Signal-to-noise ratio and noise figure	478
6.2.7	Filter implementation	405	8.2.1	Noise power density and bandwidth	479
6.3	Active-filter circuits	406	8.2.2	Signal-to-noise ratio	479
6.3.1	VCVS circuits	407	8.2.3	Noise figure	479
6.3.2	VCVS filter design using our simplified table	407	8.2.4	Noise temperature	480
6.3.3	State-variable filters	410	8.3	Bipolar transistor amplifier noise	481
6.3.4	Twin-T notch filters	414	8.3.1	Voltage noise, e_n	481
6.3.5	Allpass filters	415	8.3.2	Current noise i_n	483
6.3.6	Switched-capacitor filters	415	8.3.3	BJT voltage noise, revisited	484
6.3.7	Digital signal processing	418	8.3.4	A simple design example: loudspeaker as microphone	486
6.3.8	Filter miscellany	422	8.3.5	Shot noise in current sources and emitter followers	487
	Additional Exercises for Chapter 6	422	8.4	Finding e_n from noise-figure specifications	489
	Review of Chapter 6	423	8.4.1	Step 1: NF versus I_C	489
SEVEN: Oscillators and Timers		425	8.4.2	Step 2: NF versus R_s	489
7.1	Oscillators	425	8.4.3	Step 3: getting to e_n	490
7.1.1	Introduction to oscillators	425	8.4.4	Step 4: the spectrum of e_n	491
7.1.2	Relaxation oscillators	425	8.4.5	The spectrum of i_n	491
7.1.3	The classic oscillator–timer chip: the 555	428	8.4.6	When operating current is not your choice	491
7.1.4	Other relaxation-oscillator ICs	432	8.5	Low-noise design with bipolar transistors	492
7.1.5	Sinewave oscillators	435	8.5.1	Noise-figure example	492
7.1.6	Quartz-crystal oscillators	443	8.5.2	Charting amplifier noise with e_n and i_n	493
7.1.7	Higher stability: TCXO, OCXO, and beyond	450	8.5.3	Noise resistance	494
7.1.8	Frequency synthesis: DDS and PLL	451	8.5.4	Charting comparative noise	495
7.1.9	Quadrature oscillators	453	8.5.5	Low-noise design with BJTs: two examples	495
7.1.10	Oscillator “jitter”	457	8.5.6	Minimizing noise: BJTs, FETs, and transformers	496
7.2	Timers	457	8.5.7	A design example: 40 μ “lightning detector” preamp	497
7.2.1	Step-triggered pulses	458	8.5.8	Selecting a low-noise bipolar transistor	500
7.2.2	Monostable multivibrators	461	8.5.9	An extreme low-noise design challenge	505
7.2.3	A monostable application: limiting pulse width and duty cycle	465			

xiv	Contents	<i>Art of Electronics Third Edition</i>	
8.6	Low-noise design with JFETS	509	
8.6.1	Voltage noise of JFETS	509	
8.6.2	Current noise of JFETS	511	
8.6.3	Design example: low-noise wideband JFET “hybrid” amplifiers	512	
8.6.4	Designs by the masters: SR560 low-noise preamplifier	512	
8.6.5	Selecting low-noise JFETS	515	
8.7	Charting the bipolar–FET shootout	517	
8.7.1	What about MOSFETs?	519	
8.8	Noise in differential and feedback amplifiers	520	
8.9	Noise in operational amplifier circuits	521	
8.9.1	Guide to Table 8.3: choosing low-noise op-amps	525	
8.9.2	Power-supply rejection ratio	533	
8.9.3	Wrapup: choosing a low-noise op-amp	533	
8.9.4	Low-noise instrumentation amplifiers and video amplifiers	533	
8.9.5	Low-noise hybrid op-amps	534	
8.10	Signal transformers	535	
8.10.1	A low-noise wideband amplifier with transformer feedback	536	
8.11	Noise in transimpedance amplifiers	537	
8.11.1	Summary of the stability problem	537	
8.11.2	Amplifier input noise	538	
8.11.3	The $e_n C$ noise problem	538	
8.11.4	Noise in the transresistance amplifier	539	
8.11.5	An example: wideband JFET photodiode amplifier	540	
8.11.6	Noise versus gain in the transimpedance amplifier	540	
8.11.7	Output bandwidth limiting in the transimpedance amplifier	542	
8.11.8	Composite transimpedance amplifiers	543	
8.11.9	Reducing input capacitance: bootstrapping the transimpedance amplifier	547	
8.11.10	Isolating input capacitance: cascoding the transimpedance amplifier	548	
8.11.11	Transimpedance amplifiers with capacitive feedback	552	
8.11.12	Scanning tunneling microscope preamplifier	553	
8.11.13	Test fixture for compensation and calibration	554	
8.11.14	A final remark	555	
8.12	Noise measurements and noise sources	555	
8.12.1	Measurement without a noise source	555	
8.12.2	An example: transistor-noise test circuit	556	
8.12.3	Measurement with a noise source	556	
8.12.4	Noise and signal sources	558	
8.13	Bandwidth limiting and rms voltage measurement	561	
8.13.1	Limiting the bandwidth	561	
8.13.2	Calculating the integrated noise	563	
8.13.3	Op-amp “low-frequency noise” with asymmetric filter	564	
8.13.4	Finding the $1/f$ corner frequency	566	
8.13.5	Measuring the noise voltage	567	
8.13.6	Measuring the noise current	569	
8.13.7	Another way: roll-your-own $fA/\sqrt{\text{Hz}}$ instrument	571	
8.13.8	Noise potpourri	574	
8.14	Signal-to-noise improvement by bandwidth narrowing	574	
8.14.1	Lock-in detection	575	
8.15	Power-supply noise	578	
8.15.1	Capacitance multiplier	578	
8.16	Interference, shielding, and grounding	579	
8.16.1	Interfering signals	579	
8.16.2	Signal grounds	582	
8.16.3	Grounding between instruments	583	
	Additional Exercises for Chapter 8	588	
	Review of Chapter 8	590	
	NINE: Voltage Regulation and Power Conversion	594	
9.1	Tutorial: from zener to series-pass linear regulator	595	
9.1.1	Adding feedback	596	
9.2	Basic linear regulator circuits with the classic 723	598	
9.2.1	The 723 regulator	598	
9.2.2	In defense of the beleaguered 723	600	
9.3	Fully integrated linear regulators	600	
9.3.1	Taxonomy of linear regulator ICs	601	
9.3.2	Three-terminal fixed regulators	601	

9.3.3	Three-terminal adjustable regulators	602	9.7.1	The ac-to-dc input stage	660
9.3.4	317-style regulator: application hints	604	9.7.2	The dc-to-dc converter	662
9.3.5	317-style regulator: circuit examples	608	9.8	A real-world switcher example	665
9.3.6	Lower-dropout regulators	610	9.8.1	Switchers: top-level view	665
9.3.7	True low-dropout regulators	611	9.8.2	Switchers: basic operation	665
9.3.8	Current-reference 3-terminal regulator	611	9.8.3	Switchers: looking more closely	668
9.3.9	Dropout voltages compared	612	9.8.4	The “reference design”	671
9.3.10	Dual-voltage regulator circuit example	613	9.8.5	Wrapup: general comments on line-powered switching power supplies	672
9.3.11	Linear regulator choices	613	9.8.6	When to use switchers	672
9.3.12	Linear regulator idiosyncrasies	613	9.9	Inverters and switching amplifiers	673
9.3.13	Noise and ripple filtering	619	9.10	Voltage references	674
9.3.14	Current sources	620	9.10.1	Zener diode	674
9.4	Heat and power design	623	9.10.2	Bandgap (V_{BE}) reference	679
9.4.1	Power transistors and heatsinking	624	9.10.3	JFET pinch-off (V_P) reference	680
9.4.2	Safe operating area	627	9.10.4	Floating-gate reference	681
9.5	From ac line to unregulated supply	628	9.10.5	Three-terminal precision references	681
9.5.1	ac-line components	629	9.10.6	Voltage reference noise	682
9.5.2	Transformer	632	9.10.7	Voltage references: additional Comments	683
9.5.3	dc components	633	9.11	Commercial power-supply modules	684
9.5.4	Unregulated split supply – on the bench!	634	9.12	Energy storage: batteries and capacitors	686
9.5.5	Linear versus switcher: ripple and noise	635	9.12.1	Battery characteristics	687
9.6	Switching regulators and dc–dc converters	636	9.12.2	Choosing a battery	688
9.6.1	Linear versus switching	636	9.12.3	Energy storage in capacitors	688
9.6.2	Switching converter topologies	638	9.13	Additional topics in power regulation	690
9.6.3	Inductorless switching converters	638	9.13.1	Overvoltage crowbars	690
9.6.4	Converters with inductors: the basic non-isolated topologies	641	9.13.2	Extending input-voltage range	693
9.6.5	Step-down (buck) converter	642	9.13.3	Foldback current limiting	693
9.6.6	Step-up (boost) converter	647	9.13.4	Outboard pass transistor	695
9.6.7	Inverting converter	648	9.13.5	High-voltage regulators	695
9.6.8	Comments on the non-isolated converters	649	Review of Chapter 9		699
9.6.9	Voltage mode and current mode	651	TEN: Digital Logic		703
9.6.10	Converters with transformers: the basic designs	653	10.1	Basic logic concepts	703
9.6.11	The flyback converter	655	10.1.1	Digital versus analog	703
9.6.12	Forward converters	656	10.1.2	Logic states	704
9.6.13	Bridge converters	659	10.1.3	Number codes	705
9.7	Ac-line-powered (“offline”) switching converters	660	10.1.4	Gates and truth tables	708
			10.1.5	Discrete circuits for gates	711
			10.1.6	Gate-logic example	712
			10.1.7	Assertion-level logic notation	713
			10.2	Digital integrated circuits: CMOS and Bipolar (TTL)	714
			10.2.1	Catalog of common gates	715
			10.2.2	IC gate circuits	717
			10.2.3	CMOS and bipolar (“TTL”) characteristics	718

10.2.4	Three-state and open-collector devices	720	11.3	An example: pseudorandom byte generator	770
10.3	Combinational logic	722	11.3.1	How to make pseudorandom bytes	771
10.3.1	Logic identities	722	11.3.2	Implementation in standard logic	772
10.3.2	Minimization and Karnaugh maps	723	11.3.3	Implementation with programmable logic	772
10.3.3	Combinational functions available as ICs	724	11.3.4	Programmable logic – HDL entry	775
10.4	Sequential logic	728	11.3.5	Implementation with a microcontroller	777
10.4.1	Devices with memory: flip-flops	728	11.4	Advice	782
10.4.2	Clocked flip-flops	730	11.4.1	By <i>Technologies</i>	782
10.4.3	Combining memory and gates: sequential logic	734	11.4.2	By <i>User Communities</i>	785
10.4.4	Synchronizer	737		Review of Chapter 11	787
10.4.5	Monostable multivibrator	739			
10.4.6	Single-pulse generation with flip-flops and counters	739			
10.5	Sequential functions available as integrated circuits	740	TWELVE: Logic Interfacing		790
10.5.1	Latches and registers	740	12.1	CMOS and TTL logic interfacing	790
10.5.2	Counters	741	12.1.1	Logic family chronology – a brief history	790
10.5.3	Shift registers	744	12.1.2	Input and output characteristics	794
10.5.4	Programmable logic devices	745	12.1.3	Interfacing between logic families	798
10.5.5	Miscellaneous sequential functions	746	12.1.4	Driving digital logic inputs	802
10.6	Some typical digital circuits	748	12.1.5	Input protection	804
10.6.1	Modulo- n counter: a timing example	748	12.1.6	Some comments about logic inputs	805
10.6.2	Multiplexed LED digital display	751	12.1.7	Driving digital logic from comparators or op-amps	806
10.6.3	An n -pulse generator	752	12.2	An aside: probing digital signals	808
10.7	Micropower digital design	753	12.3	Comparators	809
10.7.1	Keeping CMOS low power	754	12.3.1	Outputs	810
10.8	Logic pathology	755	12.3.2	Inputs	812
10.8.1	dc problems	755	12.3.3	Other parameters	815
10.8.2	Switching problems	756	12.3.4	Other cautions	816
10.8.3	Congenital weaknesses of TTL and CMOS	758	12.4	Driving external digital loads from logic levels	817
	Additional Exercises for Chapter 10	760	12.4.1	Positive loads: direct drive	817
	Review of Chapter 10	762	12.4.2	Positive loads: transistor assisted	820
			12.4.3	Negative or ac loads	821
ELEVEN: Programmable Logic Devices		764	12.4.4	Protecting power switches	823
11.1	A brief history	764	12.4.5	nMOS LSI interfacing	826
11.2	The hardware	765	12.5	Optoelectronics: emitters	829
11.2.1	The basic PAL	765	12.5.1	Indicators and LEDs	829
11.2.2	The PLA	768	12.5.2	Laser diodes	834
11.2.3	The FPGA	768	12.5.3	Displays	836
11.2.4	The configuration memory	769	12.6	Optoelectronics: detectors	840
11.2.5	Other programmable logic devices	769			
11.2.6	The software	769			

12.6.1	Photodiodes and phototransistors	841	13.2.8	PWM as digital-to-analog converter	888
12.6.2	Photomultipliers	842	13.2.9	Frequency-to-voltage converters	890
12.7	Optocouplers and relays	843	13.2.10	Rate multiplier	890
12.7.1	I: Phototransistor output optocouplers	844	13.2.11	Choosing a DAC	891
12.7.2	II: Logic-output optocouplers	844	13.3	Some DAC application examples	891
12.7.3	III: Gate driver optocouplers	846	13.3.1	General-purpose laboratory source	891
12.7.4	IV: Analog-oriented optocouplers	847	13.3.2	Eight-channel source	893
12.7.5	V: Solid-state relays (transistor output)	848	13.3.3	Nanoamp wide-compliance bipolarity current source	894
12.7.6	VI: Solid-state relays (triac/SCR output)	849	13.3.4	Precision coil driver	897
12.7.7	VII: ac-input optocouplers	851	13.4	Converter linearity – a closer look	899
12.7.8	Interrupters	851	13.5	Analog-to-digital converters	900
12.8	Optoelectronics: fiber-optic digital links	852	13.5.1	Digitizing: aliasing, sampling rate, and sampling depth	900
12.8.1	TOSLINK	852	13.5.2	ADC Technologies	902
12.8.2	Versatile Link	854	13.6	ADCs I: Parallel (“flash”) encoder	903
12.8.3	ST/SC glass-fiber modules	855	13.6.1	Modified flash encoders	903
12.8.4	Fully integrated high-speed fiber-transceiver modules	855	13.6.2	Driving flash, folding, and RF ADCs	904
12.9	Digital signals and long wires	856	13.6.3	Undersampling flash-converter example	907
12.9.1	On-board interconnections	856	13.7	ADCs II: Successive approximation	908
12.9.2	Intercard connections	858	13.7.1	A simple SAR example	909
12.10	Driving Cables	858	13.7.2	Variations on successive approximation	909
12.10.1	Coaxial cable	858	13.7.3	An A/D conversion example	910
12.10.2	The right way – I: Far-end termination	860	13.8	ADCs III: integrating	912
12.10.3	Differential-pair cable	864	13.8.1	Voltage-to-frequency conversion	912
12.10.4	RS-232	871	13.8.2	Single-slope integration	914
12.10.5	Wrapup	874	13.8.3	Integrating converters	914
Review of Chapter 12		875	13.8.4	Dual-slope integration	914
			13.8.5	Analog switches in conversion applications (a detour)	916
THIRTEEN : Digital meets Analog		879	13.8.6	Designs by the masters: Agilent’s world-class “multislope” converters	918
13.1	Some preliminaries	879	13.9	ADCs IV: delta–sigma	922
13.1.1	The basic performance parameters	879	13.9.1	A simple delta–sigma for our suntan monitor	922
13.1.2	Codes	880	13.9.2	Demystifying the delta–sigma converter	923
13.1.3	Converter errors	880	13.9.3	$\Delta\Sigma$ ADC and DAC	923
13.1.4	Stand-alone versus integrated	880	13.9.4	The $\Delta\Sigma$ process	924
13.2	Digital-to-analog converters	881	13.9.5	An aside: “noise shaping”	927
13.2.1	Resistor-string DACs	881	13.9.6	The bottom line	928
13.2.2	$R-2R$ ladder DACs	882	13.9.7	A simulation	928
13.2.3	Current-steering DACs	883	13.9.8	What about DACs?	930
13.2.4	Multiplying DACs	884			
13.2.5	Generating a voltage output	885			
13.2.6	Six DACs	886			
13.2.7	Delta–sigma DACs	888			

13.9.9	Pros and Cons of $\Delta\Sigma$ oversampling converters	931	13.14.8	A “hybrid digital filter”	983
13.9.10	Idle tones	932		Additional Exercises for Chapter 13	984
13.9.11	Some delta–sigma application examples	932		Review of Chapter 13	985
13.10	ADCs: choices and tradeoffs	938	FOURTEEN: Computers, Controllers, and Data Links 989		
13.10.1	Delta–sigma and the competition	938	14.1	Computer architecture: CPU and data bus	990
13.10.2	Sampling versus averaging ADCs: noise	940	14.1.1	CPU	990
13.10.3	Micropower A/D converters	941	14.1.2	Memory	991
13.11	Some unusual A/D and D/A converters	942	14.1.3	Mass memory	991
13.11.1	ADE7753 multifunction ac power metering IC	943	14.1.4	Graphics, network, parallel, and serial ports	992
13.11.2	AD7873 touchscreen digitizer	944	14.1.5	Real-time I/O	992
13.11.3	AD7927 ADC with sequencer	945	14.1.6	Data bus	992
13.11.4	AD7730 precision bridge-measurement subsystem	945	14.2	A computer instruction set	993
13.12	Some A/D conversion system examples	946	14.2.1	Assembly language and machine language	993
13.12.1	Multiplexed 16-channel data-acquisition system	946	14.2.2	Simplified “x86” instruction set	993
13.12.2	Parallel multichannel successive-approximation data-acquisition system	950	14.2.3	A programming example	996
13.12.3	Parallel multichannel delta–sigma data-acquisition system	952	14.3	Bus signals and interfacing	997
13.13	Phase-locked loops	955	14.3.1	Fundamental bus signals: data, address, strobe	997
13.13.1	Introduction to phase-locked loops	955	14.3.2	Programmed I/O: data out	998
13.13.2	PLL components	957	14.3.3	Programming the XY vector display	1000
13.13.3	PLL design	960	14.3.4	Programmed I/O: data in	1001
13.13.4	Design example: frequency multiplier	961	14.3.5	Programmed I/O: status registers	1002
13.13.5	PLL capture and lock	964	14.3.6	Programmed I/O: command registers	1004
13.13.6	Some PLL applications	966	14.3.7	Interrupts	1005
13.13.7	Wrapup: noise and jitter rejection in PLLs	974	14.3.8	Interrupt handling	1006
13.14	Pseudorandom bit sequences and noise generation	974	14.3.9	Interrupts in general	1008
13.14.1	Digital-noise generation	974	14.3.10	Direct memory access	1010
13.14.2	Feedback shift register sequences	975	14.3.11	Summary of PC104/ISA 8-bit bus signals	1012
13.14.3	Analog noise generation from maximal-length sequences	977	14.3.12	The PC104 as an embedded single-board computer	1013
13.14.4	Power spectrum of shift-register sequences	977	14.4	Memory types	1014
13.14.5	Low-pass filtering	979	14.4.1	Volatile and non-volatile memory	1014
13.14.6	Wrapup	981	14.4.2	Static versus dynamic RAM	1015
13.14.7	“True” random noise generators	982	14.4.3	Static RAM	1016
			14.4.4	Dynamic RAM	1018
			14.4.5	Nonvolatile memory	1021
			14.4.6	Memory wrapup	1026
			14.5	Other buses and data links: overview	1027
			14.6	Parallel buses and data links	1028
			14.6.1	Parallel chip “bus” interface – an example	1028

14.6.2	Parallel chip data links – two high-speed examples	1030	15.7	Design example 5: stabilized mechanical platform	1077
14.6.3	Other parallel computer buses	1030	15.8	Peripheral ICs for microcontrollers	1078
14.6.4	Parallel peripheral buses and data links	1031	15.8.1	Peripherals with direct connection	1079
14.7	Serial buses and data links	1032	15.8.2	Peripherals with SPI connection	1082
14.7.1	SPI	1032	15.8.3	Peripherals with I ² C connection	1084
14.7.2	I ² C 2-wire interface (“TWT”)	1034	15.8.4	Some important hardware constraints	1086
14.7.3	Dallas–Maxim “1-wire” serial interface	1035	15.9	Development environment	1086
14.7.4	JTAG	1036	15.9.1	Software	1086
14.7.5	Clock-be-gone: clock recovery	1037	15.9.2	Real-time programming constraints	1088
14.7.6	SATA, eSATA, and SAS	1037	15.9.3	Hardware	1089
14.7.7	PCI Express	1037	15.9.4	The Arduino Project	1092
14.7.8	Asynchronous serial (RS-232, RS-485)	1038	15.10	Wrapup	1092
14.7.9	Manchester coding	1039	15.10.1	How expensive are the tools?	1092
14.7.10	Biphase coding	1041	15.10.2	When to use microcontrollers	1093
14.7.11	RLL binary: bit stuffing	1041	15.10.3	How to select a microcontroller	1094
14.7.12	RLL coding: 8b/10b and others	1041	15.10.4	A parting shot	1094
14.7.13	USB	1042		Review of Chapter 15	1095
14.7.14	FireWire	1042			
14.7.15	Controller Area Network (CAN)	1043	APPENDIX A: Math Review		1097
14.7.16	Ethernet	1045	A.1	Trigonometry, exponentials, and logarithms	1097
14.8	Number formats	1046	A.2	Complex numbers	1097
14.8.1	Integers	1046	A.3	Differentiation (Calculus)	1099
14.8.2	Floating-point numbers	1047	A.3.1	Derivatives of some common functions	1099
	Review of Chapter 14	1049	A.3.2	Some rules for combining derivatives	1100
			A.3.3	Some examples of differentiation	1100
FIFTEEN: Microcontrollers		1053			
15.1	Introduction	1053	APPENDIX B: How to Draw Schematic Diagrams		1101
15.2	Design example 1: suntan monitor (V)	1054	B.1	General principles	1101
15.2.1	Implementation with a microcontroller	1054	B.2	Rules	1101
15.2.2	Microcontroller code (“firmware”)	1056	B.3	Hints	1103
15.3	Overview of popular microcontroller families	1059	B.4	A humble example	1103
15.3.1	On-chip peripherals	1061			
15.4	Design example 2: ac power control	1062	APPENDIX C: Resistor Types		1104
15.4.1	Microcontroller implementation	1062	C.1	Some history	1104
15.4.2	Microcontroller code	1064	C.2	Available resistance values	1104
15.5	Design example 3: frequency synthesizer	1065	C.3	Resistance marking	1105
15.5.1	Microcontroller code	1067	C.4	Resistor types	1105
15.6	Design example 4: thermal controller	1069	C.5	Confusion derby	1105
15.6.1	The hardware	1070			
15.6.2	The control loop	1074	APPENDIX D: Thévenin’s Theorem		1107
15.6.3	Microcontroller code	1075	D.1	The proof	1107

D.1.1	Two examples – voltage dividers	1107	I.3	Recording analog-format broadcast or cable television	1135
D.2	Norton’s theorem	1108	I.4	Digital television: what is it?	1136
D.3	Another example	1108	I.5	Digital television: broadcast and cable delivery	1138
D.4	Millman’s theorem	1108	I.6	Direct satellite television	1139
APPENDIX E: LC Butterworth Filters		1109	I.7	Digital video streaming over internet	1140
E.1	Lowpass filter	1109	I.8	Digital cable: premium services and conditional access	1141
E.2	Highpass filter	1109	I.8.1	Digital cable: video-on-demand	1141
E.3	Filter examples	1109	I.8.2	Digital cable: switched broadcast	1142
APPENDIX F: Load Lines		1112	I.9	Recording digital television	1142
F.1	An example	1112	I.10	Display technology	1142
F.2	Three-terminal devices	1112	I.11	Video connections: analog and digital	1143
F.3	Nonlinear devices	1113	APPENDIX J: SPICE Primer		1146
APPENDIX G: The Curve Tracer		1115	J.1	Setting up ICAP SPICE	1146
APPENDIX H: Transmission Lines and Impedance Matching		1116	J.2	Entering a Diagram	1146
H.1	Some properties of transmission lines	1116	J.3	Running a simulation	1146
H.1.1	Characteristic impedance	1116	J.3.1	Schematic entry	1146
H.1.2	Termination: pulses	1117	J.3.2	Simulation: frequency sweep	1147
H.1.3	Termination: sinusoidal signals	1120	J.3.3	Simulation: input and output waveforms	1147
H.1.4	Loss in transmission lines	1121	J.4	Some final points	1148
H.2	Impedance matching	1122	J.5	A detailed example: exploring amplifier distortion	1148
H.2.1	Resistive (lossy) broadband matching network	1123	J.6	Expanding the parts database	1149
H.2.2	Resistive attenuator	1123	APPENDIX K: “Where Do I Go to Buy Electronic Goodies?”		1150
H.2.3	Transformer (lossless) broadband matching network	1124	APPENDIX L: Workbench Instruments and Tools		1152
H.2.4	Reactive (lossless) narrowband matching networks	1125	APPENDIX M: Catalogs, Magazines, Databooks		1153
H.3	Lumped-element delay lines and pulse-forming networks	1126	APPENDIX N: Further Reading and References		1154
H.4	Epilogue: ladder derivation of characteristic impedance	1127	APPENDIX O: The Oscilloscope		1158
H.4.1	First method: terminated line	1127	O.1	The analog oscilloscope	1158
H.4.2	Second method: semi-infinite line	1127	O.1.1	Vertical	1158
H.4.3	Postscript: lumped-element delay lines	1128	O.1.2	Horizontal	1158
APPENDIX I: Television: A Compact Tutorial		1131	O.1.3	Triggering	1159
I.1	Television: video plus audio	1131	O.1.4	Hints for beginners	1160
I.1.1	The audio	1131	O.1.5	Probes	1160
I.1.2	The video	1132	O.1.6	Grounds	1161
I.2	Combining and sending the audio + video: modulation	1133	O.1.7	Other analog scope features	1161
			O.2	The digital oscilloscope	1162

O.2.1	What's different?	1162	APPENDIX P: Acronyms and Abbreviations	1166
O.2.2	Some cautions	1164	Index	1171

LIST OF TABLES

1.1. Representative Diodes.	32	8.4. Noise Integrals.	564
2.1. Representative Bipolar Transistors.	74	8.5. Auto-zero Noise Measurements.	569
2.2. Bipolar Power Transistors.	106	9.1. 7800-style Fixed Regulators.	602
3.1. JFET Mini-table.	141	9.2. Three-terminal Adjustable Voltage Regulators (LM317-style).	605
3.2. Selected Fast JFET-input Op-amps.	155	9.3. Low-dropout Linear Voltage Regulators.	614
3.3. Analog Switches.	176	9.4. Selected Charge-pump Converters.	640
3.4a. MOSFETs – Small n -channel (to 250 V), and p -channel (to 100 V).	188	9.5a. Voltage-mode Integrated Switching Regulators.	653
3.4b. n -channel Power MOSFETs, 55 V to 4500 V.	189	9.5b. Selected Current-mode Integrated Switching Regulators.	654
3.5. MOSFET Switch Candidates.	206	9.6. External-switch Controllers.	658
3.6. Depletion-mode n -channel MOSFETs.	210	9.7. Shunt (2-terminal) Voltage References.	677
3.7. Junction Field-Effect Transistors (JFETs).	217	9.8. Series (3-terminal) Voltage References.	678
3.8. Low-side MOSFET Gate Drivers.	218	9.9. Battery Choices.	689
4.1. Op-amp Parameters.	245	9.10. Energy Storage: Capacitor Versus Battery.	690
4.2a. Representative Operational Amplifiers.	271	10.1. Selected Logic Families.	706
4.2b. Monolithic Power and High-voltage Op-amps.	272	10.2. 4-bit Signed Integers in Three Systems of Representation.	707
5.1. Millivoltmeter Candidate Op-amps.	296	10.3. Standard Logic Gates.	716
5.2. Representative Precision Op-amps.	302	10.4. Logic Identities.	722
5.3. Eight Low-input-current Op-amps.	303	10.5. Selected Counter ICs.	742
5.4. Representative High-speed Op-amps.	310	10.6. Selected Reset/Supervisors.	756
5.5. “Seven” Precision Op-amps: High Voltage.	320	12.1. Representative Comparators.	812
5.6. Chopper and Auto-zero Op-amps.	335	12.2. Comparators.	813
5.7. Selected Difference Amplifiers.	353	12.3. Power Logic Registers.	819
5.8. Selected Instrumentation Amplifiers	363	12.4. A Few Protected MOSFETs.	825
5.9. Selected Programmable-gain Instrumentation Amplifiers.	370	12.5. Selected High-side Switches.	826
5.10. Selected Differential Amplifiers.	375	12.6. Selected Panel-mount LEDs.	832
6.1. Time-domain Performance Comparison for Lowpass Filters.	406	13.1. Six Digital-to-analog Converters.	889
6.2. VCVS Lowpass Filters.	408	13.2. Selected Digital-to-analog Converters.	893
7.1. 555-type Oscillators.	430	13.3. Multiplying DACs.	894
7.2. Oscillator Types.	452	13.4. Selected Fast ADCs.	905
7.3. Monostable Multivibrators.	462	13.5. Successive-approximation ADCs.	910
7.4. “Type 123” Monostable Timing.	463	13.6. Selected Micropower ADCs.	916
8.1a. Low-noise Bipolar Transistors (BJTs).	501	13.7. 4053-style SPDT Switches.	917
8.1b. Dual Low-noise BJTs.	502	13.8. Agilent’s Multislope III ADCs.	921
8.2. Low-noise Junction FETs (JFETs).	516	13.9. Selected Delta–sigma ADCs.	935
8.3a. Low-noise BJT-input Op-amps.	522	13.10. Audio Delta–sigma ADCs.	937
8.3b. Low-noise FET-input Op-amps.	523	13.11. Audio ADCs.	939
8.3c. High-speed Low-noise Op-amps.	524	13.12. Speciality ADCs.	942

13.13. Phase-locked Loop ICs.	972	14.3. Common Buses and Data Links.	1029
13.14. Single-tap LFSRs.	976	14.4. RS-232 Signals.	1039
13.15. LFSRs with Length a Multiple of 8.	976	14.5. ASCII Codes.	1040
14.1. Simplified x86 Instruction Set.	994	C.1. Selected Resistor Types.	1106
14.2. PC104/ISA Bus Signals.	1013	E.1. Butterworth Lowpass Filters.	1110
		H.1. Pi and T Attenuators.	1124