

Subject Index

- 1-wire bus, *see* computer, data bus
- 1T1C cell, 1022
- 2's complement, *see* number, codes
- 6T cell, 1019
- 8b/10b code, 1044

- 8051, *see* microcontroller

- abbreviations, 1170
- ABEL, *see* programmable logic device (PLD)
- absolute-value circuit, 257
- abuse, *see* argument
- ac power control
 - microcontroller, **1065–1068**
- ac powered
 - dc power supply topologies, 630
- academics, 332n
- acceleration
 - algorithm, 1072
- accelerometer, *see* sensor
- acoustic ranging, 207
- acronyms, 1170
- active-HIGH, active-LOW, *see* logic, 704
- Adafruit, 1085, 1099r
- ADC, *see also* converter, AD/DA, 881, **902–957**, 1056, 1064, 1073, 1074, 1085, 1091, 1099r
 - ac monitor, **945**
 - analog switches in, 918
 - application examples, 909, 912, 934, 938, 948, 989r
 - bridge-sensor oriented, 947, 949
 - charge redistribution, 911, 952n
 - choosing, **940**, 989r
 - comparison, **940**
 - data-acquisition system (DAQ), **948–957**
 - isolated SPI, 952
 - multiplexed 16-channel SAR, **948ff**, 950
 - parallel 8-channel $\Delta\Sigma$, **954**, 956
 - parallel 8-channel SAR, **952**, 953–955
 - delta-sigma, *see* delta-sigma
 - differential-input, 374, 380, 382
 - flash, 904, 905, **905–910**, 988r
 - driving (design example), 908, 906–909
 - folding, 906
 - for thermocouple, 1087
 - half-flash, 905
 - integrating, **914–940**
 - as lowpass filter, 942
 - dual-slope, 904, **916ff**, 917, 988r
 - multislope, 904, 921, 923t, **920–924**
 - normal-mode rejection, 917
 - powerline rejection, 917, 921
 - single-slope, 904, 916, **916**, 988r
 - introduction, 881–883
 - low-power shootout, 943
 - micropower, 918t, 943
 - noise
 - filtering out-of-band, 913
 - sampling vs integrating, **942**
 - parallel, **905–910**
 - pipelined, 906
 - pipelined flash, 905
 - precision, in microcontroller, 1074
 - resolution
 - effective, 937n
 - noise-free, 937n
 - RF
 - driving (design example), 908, 906–909
 - selected, 907t
 - sequencer, 947
 - shootout, 941t
 - ADCs, SAR vs $\Delta\Sigma$, 941
 - specialty, 944, 944t
 - subsystem, 1087
 - successive approximation, 904, 910, 910s, 912t, **910–914**, 988r
 - block diagram, 913
 - design example, 914, 912–914
 - SPI timing, 913
 - system design examples, **948–957**
- tables, 907t, 912t, 918t, 923t, 939t, 941t, 944t
- techniques, 904
- timing example, 1092, 1092g
 - pseudocode, 1093
- touchscreen digitizer, 946
- tracking, 911
- transformer input coupling, 382
- undersampling
 - deliberate, 909
- V to f , 434, 904, **914ff**, 988r
 - nonlinearity, 916g
- adder, *see* logic
- admittance, 69, 90n

- alias, *see also* filter, 395, 903, 933g
 - digital oscilloscope, 442n, 1168
 - in switched-capacitor filter, 417
 - undersampling conversion, 909
- AM radio, 55, 56s
 - waveform, 55g
 - waveforms, 56s
- amp, 2
- amplifier
 - clamping output, 383
- amplifier
 - autonulling, 298
 - autonulling (design example), 297
 - input errors, 306
 - balanced audio, 376
 - class-A, 106n, 107
 - class-AB, 108, 108
 - class-B, 107n
 - distortion, 309
 - class-D, 109, 109s, 673
 - CMRR, 347ff
 - common-base, 91, 549, 549
 - common-emitter, 87ff, 91, 128r
 - biasing, 95, 96ff
 - bootstrapping, 112
 - bypassed emitter resistor, 96
 - distortion, 95s
 - emitter resistor as feedback, 96
 - gain of, 93
 - input impedance of, 95
 - maximum gain of, 98
 - nonlinearity, 94, 94–96s
 - revisited (Ebers-Moll), 93
 - composite, 332, 333, 365, 543–547, 922, 922
 - slew rate of, 922
 - vs single-stage, 546
 - current, *see* transimpedance amplifier
 - current-feedback, 378, 513
 - current-sensing, 278
 - difference, 348, 347–387, 390r
 - applications, 349ff
 - as current source, 350, 351
 - bandwidth, 355
 - BJT, 102ff
 - CMRR, 355g
 - CMRR trim, 356, 357
 - common-mode input range, 354
 - configurations, 356
 - current sensing, 349, 350
 - filter node, 355
 - ground-loop isolation, 349, 350, 584
 - input impedance, 352, 354
 - line driver, 351
 - offset trim, 355, 357
 - performance parameters, 352ff
 - tricks, 349
 - differential, 115, 129r, 373ff, 375t, 347–387, 390r, 1073
 - as comparator, 105
 - as dc amplifier, 104
 - bandwidth, 385
 - bias pin, 378
 - biasing, 104
 - BJT, 102ff
 - choosing, 383ff
 - CMRR, 347, 376, 384
 - common-mode input range, 378, 381, 384
 - common-mode output impedance, 379
 - common-mode output voltage, 380
 - compensation, 378
 - current-mirror load, 105, 105, 153, 496
 - distortion, 386, 386g
 - filtering, 385
 - gain of, 103
 - gain setting, 384
 - gain-setting resistor, 378
 - input impedance, 384
 - input impedance matching, 382
 - input impedance of, 376
 - JFET, 152ff
 - no Miller effect in, 114
 - noise, 386, 496, 520
 - offset voltage, 384
 - output voltage, 383
 - phase splitter, 105
 - settling time, 385
 - single-ended output, 377
 - slew rate, 385
 - speed, 385
 - supply voltage, 383
 - use with ADCs, 380, 382
 - use with single-ended input, 376
 - distortion
 - barn-roof, 95
 - SPICE simulation, 1152
 - equalization, 380, 381
 - error, 598, 604 (box), 642, 699, 700r
 - in linear regulator, 597
 - in switchmode regulator, 646, 651
 - fully differential, *see* amplifier, differential

- funnel, 376n
- gain
 - predictability of, 117
- general purpose, 274
- grounded-base, 115
- grounded-emitter, 94
- high voltage, 696
- hybrid
 - low-noise, 534
- input errors, 301, 388r
- input impedance
 - effect of feedback on, 118
- input protection, 210
- instrumentation, *see* instrumentation amplifier
- isolation, **585ff**
 - capacitive, 586
- JFET, **146ff**
 - differential, 152
 - low noise, **509–520**
 - op-amp hybrid, 151, 153g, 155g, 343, 344, 534
 - series-feedback pair, 150, 151g
 - with cascode, 148
- laboratory, 298
- laboratory, general-purpose, 274
- logarithmic, *see* AoE 2nd ed., pp 212–216
- low-noise, 496, 498, 500, 505, 506
- MOSFET power, 221r
- noise, *see also* noise, 481
 - in inverting amplifier, 521
 - in noninverting amplifier, 520
 - measurement, **555ff**
 - total, vs R_s , 526g
 - total, vs frequency, 531g
- noise model, 481, 492
- op-amp, *see* op-amp
 - BJT hybrid, 534
 - JFET hybrid, 153g, 534, 545
 - low-noise, 522–524t
 - low-noise, choosing, **525–533**
 - single-supply, 261
- operational transconductance, *see* OTA (operational transconductance amplifier)
- output errors, 307
- output impedance
 - effect of feedback on, 119
 - inductive, 120n
- patch clamp, 552
- peaking, 152, 153g, 154, 154g, 378, 385, 385g
- photodiode, 233, 547, 548
- photomultiplier, 872
- piezo, 208, 209
- programmable gain (PGA), 948
- programmable-gain (PGA), **370**, 370, 371t
- sense, 1019, 1021
- STM, 553
- summing, 234
- switchable gain, 182
- switching, 109, 109s, 673
- transformer in feedback, 285, 536
- transimpedance, *see* transimpedance amplifier
- video and RF, 274, 533
- voltage-feedback, 378
- wideband analog link, 352, 380
- world's quietest, 505, 507g, 508t
- amplitude
 - modulation, *see* modulation
 - rms, 14
- analog
 - vs digital, 703
- analog switch, 176t
 - 4053-style, 918ff, 919t
 - charge injection, 176t, 180, 181g
 - vs R_{ON} , 182g
- FET, **171–184**
 - applications, 182–184
 - capacitance, 178–181
 - charge injection, 180
 - CMOS, 172
 - feedthrough, 179g
 - gate drive, 173
 - JFET, 172
 - latchup, 174
 - limitations, 174
 - multiplexer, 173
 - ON resistance, 171, 172, 173g, 177g, 178g, 175–178
 - protected, 175
 - speed, 178
 - substrate effects, 173n
 - T-switch, 179
 - in ADCs, **918ff**
 - in conversion applications, **918ff**
 - logic-family, 918ff
 - transmission gate, *see* logic
- analog-to-digital, *see* ADC
- anti-alias, *see* filter
- antisaturation circuit, 717n, 812
- aperture time, 942
- apodization, 420
- arbitrary function generator, 18

- Arduino, *see also* microcontroller, 1056, 1091n, **1096**, 1098, 1099, 1100r
 argument, *see also* abuse, *see* computer, 996
 immediate, 996
 ARM, *see* microcontroller
 Armstrong, Edwin, 971n
 Art of Electronics
 logo wristwatch, 448p
 ASCII, 706
 ASCII code, 1042, 1043t
 ASIC, 714, 777, 787, 788r
 assertion-level logic, 713
 assign
 in Verilog, 777
 ASSP, 714, 788r, 1034, 1097
 asynchronous, *see also* memory, *see* logic, 1019
 communication, 771
 RS-232, **1041ff**
 ATSC, 1137, 1141n
 attenuator, 17
 digital, 1070
 matched impedance, 1127, 1128t
 audio
 analog, 1135
 balanced driver, 351, 351, 376, 380, 383
 balanced impedances, 355n
 balanced line, 348
 digital, 1135
 sampling rate, 904
 autocorrelation
 of LSFR, 979
 of PRBS, 980g
 autozero, *see* op-amp
 avalanche
 see MOSFET, 1
 AVR, *see* microcontroller

 bandgap, *see* voltage reference
 bandwidth
 limit, 1166, 1169
 narrowing, **574ff**
 lock-in detection, 398, 563, 576, **575–578**, 593r, 847
 lock-in modulation, 577
 modulation feedthrough, 577
 synchronous detection, 847
 of difference amplifier, 355
 of noise, 477
 of op-amp, 308
 signal averaging, 576

 bang–bang control, 608, 644n, 645, 645, 649, 650, 700r, 1073
 base
 spreading resistance, *see* r_{bb}
 baseband, 395
 BASIC
 Stamp, 1091
 battery, 2, 9, **686ff**, 688p
 alkaline, 196n, 753
 backup, 36
 characteristics, 687, 689t
 choosing, 688
 Diehard, 985
 discharge curves, 687g
 energy density
 vs capacitor, 690g
 energy storage
 vs capacitor, 690t
 Li-ion
 charging, 688
 power density
 vs capacitor, 690g
 primary, 686
 choices, 687
 rechargeable, *see* battery, secondary
 secondary, 686
 charging, 687
 choices, 687
 series resistance of, 8
 baud, 866
 Baudot, 708
 BCD, *see* number
 BeagleBoard, 1056n
 bench instrument favorites, 1156
 beta, *see* BJT
 BGA, 789r
 bias
 tee, 835
 biasing
 bad, 85, 125
 of emitter follower, 83
 with compensated V_{BE} drop, 97
 with dc feedback, 98
 with LED, 86n
 bibliography, **1158ff**
 bifilar, 656n
 binary
 number, *see* number
 search, 910
 biology

- electrical engineer's view of, 805
- biphase code, 1044, 1044
- bipolar transistor, *see* BJT
- bit
- effective number of, 930, 931g
 - error rate, 977
 - grooming, 1142n
 - scrambling, 977
- bit stuffing, 1044
- bitstream, *see* delta-sigma
- BJT (bipolar junction transistor), **71ff**
- active ballasting, 113
 - amplifier building blocks, 105ff
 - as transconductance amplifier, 90
 - base resistance, *see* r_{bb}
 - basic circuit topologies, 90
 - basic circuits, 91
 - beta, 72, 74g, 501, 502t
 - collector output resistance, 93n
 - current noise, 483, 493g
 - vs current, 484g
 - vs frequency, 484g
 - current ratio, 102g
 - current sharing in, 112
 - current source, 128r
 - Darlington, **109ff**, 129r, 610, 752, 817, 1084
 - beta vs current, 110g
 - complementary, *see* Sziklai connection
 - saturation, 752, 752
 - Early effect, *see* Early effect
 - Ebers–Moll model, 127r
 - Ebers–Moll model, 90
 - emitter follower, *see* emitter follower, 128r
 - emitter impedance of, 92
 - gain-bandwidth product, 549g
 - I_C vs V_{CE} , 92
 - improved model, 90ff
 - inductive load, 74
 - LED driver, 76
 - logic with, 123
 - low-noise, 501t
 - challenge, **505ff**
 - replace with JFET, 500
 - selecting, **500–505**, 507
 - low-noise amplifier, *see also* amplifier, 495, 496, 498, 500, 505, 506
 - challenge, 507g, 508t
 - low-noise design with, **492–509**
 - example, 495
 - low-noise dual, 502t
 - manufacturing spread, 508g
 - noise, **481ff**, 591, 592r
 - from NF, 489–492
 - measuring, 508
 - model, 481, 488
 - resistance, 494
 - test circuit, 557
 - vs JFET, 517
 - noise resistance, *see* noise resistance
 - operating modes, 126r
 - paralleling, 112
 - pin labels, 126r
 - pinouts, 72, 502
 - polarities, 126r
 - power, 106t
 - pulse generator, 458, 459s
 - r_{bb} , **481ff**, 483g, 501, 502t, 503, 505ff, 535
 - representative, 74t
 - rules of thumb, 91, 127r
 - saturation current, I_S , 91
 - series connection of, 697
 - simple model, 72
 - limitations of, 90
 - single-stage voltage gain, 93n, 98, 105n
 - superbeta, 111, 252, 303t, 323, 326
 - switch, 73ff, 91, 126, 127r
 - Sziklai connection, **110ff**, 111, 129r, 148, 207, 214n, 229, 600n, 610
 - table of, 74t, 106t, 501, 502t
 - terminal notation, 71
 - transconductance, 126, 127r
 - V_{BE} spread, 508g
 - V_{BE} tempco, 92
 - voltage noise, **481ff**, 493g
 - calculation (circuit example), 486
 - charting, **493ff**, 494, 495g, 504g
 - figure of merit, 505n
 - from i_n through R_s , 483
 - vs r_{bb} , 483g
 - vs current, 481–483g, 485, 486g
 - vs frequency, 485, 486g, 504g, 519g
 - vs power MOSFET and IGBT, 201, 202t, 208t
- Black, Harold, *see also* feedback, 116, 118
- Blackman's impedance relation, 120
- Blackman-Harris, *see* window, sampling
- Blu-ray, 703n, 847, 995, 1139
- Bluetooth, 1056, 1064, 1080
- Bode plot, 247g, 281g, **280–285**, 311g, 901, 963g, 965g
- boost, *see* switchmode
- bootstrap, **111ff**

- cascode, in TIA, 550
- leakage cancelation, capacitor, 899
- of capacitor, 682, 683
- of collector load, 112
- of guard shield, 359, 548, 587
- of JFET drain, 343, 344
- of op-amp follower, 233
- of power supply, 359
- of TIA, 547, 550
- twin-T filter, 414
- bounce, *see* switch
- boxcar integration, *see* bandwidth, narrowing
- branch
 - you're sitting on, sawing off, 1095
- breakdown, *see also* second breakdown, 627
 - base-emitter, 82
 - MOSFET gate, 199
- brickwall, *see* filter
- brownout, 1067
- buck, *see* switchmode
- buffer
 - logic, 23, 218t
 - unity-gain, 275, 311, 840
- burn-in, 683
- burst mode, 643n
- bus, *see also* computer, 1032t
 - multidrop, 993
 - point-to-point, 993
- byte, 706, 993
- cable
 - cat-5, 352, 380, 381, 859, 1121
 - cat-6, 352, 859
 - coax, 380, **1120–1126**
 - counterwound helix, 1134p, 1134s
 - driving with logic, 853, 854s, 854s, 855, 855s, 856, 856s, 857, 857s, 858s, **852–859**, 1124
 - driving with video, 857
 - pre-emphasis, 858
 - reflections, 853, 854s, 854s, 855, 855s, 856, 856s, 857, 857s, 858s, **852–859**, 1120g, 1122, 1123s
 - terminating, 853, 854s, 855, 855s, 856, 856s, 857, 857s, 858s, **852–859**, **1121ff**
 - video, 1144
 - differential, **859–864**
 - digital signals through, **850ff**, 879r
 - driving, **850ff**, 879r
 - equalization, 858
 - pre-emphasis, 858
 - shielded, *see also* cable, coax, 587
 - STP, 859
 - television, 1138
 - terminated
 - capacitance disappears, 854
 - termination
 - back, 739, **857**, **1122**, 1126
 - double-ended, **856**, 1126
 - far end, **854**
 - series, 739, **857**, **1122**
 - twisted-pair, **859–864**
 - UTP, 352, 859
- calculus, 1103
- calibration
 - data in EEPROM, 1070
- CALL, 999
- CAN bus, *see also* computer, data bus, 1046, **1046ff**, 1047, 1064, 1084
 - isolated, 1048
 - levels, 1047
- capacitance
 - disappears in terminated cable, 854, 1120
 - feedback, *see also* Miller effect, 113
 - gate, 197g, **197**
 - junction, 114
 - multiplier, 537, 557, 578, 579g
 - of analog switch, 178–181
 - of op-amp, 532
 - sensor, 1090
- capacitive
 - coupling, 581
 - isolator, 586
- capacitor, **18ff**, 20p, 68r
 - air, 326
 - as microphone, 682n
 - blocking, 19, 43, 69r
 - in H-bridge, 659
 - bootstrap to suppress leakage, 682, 683
 - bypass, 19, 54, 69r, 758, 759, 851, 852, 1059
 - resonances, 851n
 - ceramic, 438
 - ESR and stability, 561, 617n
 - compensation, 283, 700r
 - current through, 19, 46
 - dielectric absorption, 28, **300**, 301g, 326, 388r, 422, 917, 922
 - digital, 1085
 - electrolytic, 20p, 232n, 301g, 393, 579, 599, 633ff, 661, 690t, 851
 - dc coupling eliminates, 496

- energy density
 - vs battery, 690g
 - energy storage
 - vs battery, 690t
 - energy storage in, 19, 671, 688
 - ESL, 28, 646
 - ESR, 28, 561, 599n, 611, 646, 671, 689
 - filter attenuation, effect on, 393g
 - increased ripple from, 639n
 - film, 19, 20p, 279, 300, 326, 422, 438, 631p
 - flying
 - driving MOSFETs, 822, 843
 - in power conversion, 184, 638ff
 - HV discharge circuit, 211
 - international notation, 5n
 - leakage, 300
 - bootstrap cure, 899
 - leakage compensation, 298
 - Miller, 282, 283, 597
 - multiplier, *see* capacitance
 - mylar, 19, 20p
 - non-ideal, 28, 388r
 - in filter, 392
 - parallel, 21
 - piezoelectric effect in, 682n
 - power density
 - vs battery, 690g
 - powerline rated, 631, 631p, 664p, 668, 671
 - discharge resistor, 632
 - RC circuit, 21
 - reactance of, 42, 45, 49g
 - reactive current, 47g
 - ripple current, *see also* current, 634, 635s, 659
 - series, 21
 - speedup, 74n, 808s
 - storage, 32, 55, 69r, 665, 699r
 - ripple current, 634
 - storage, in power supply, 633
 - surface-mount, 20p, 65, 66p, 758, 759
 - switched, *see* filter, switched-capacitor
 - switched, filter, 415ff, 436
 - timing, 55, 69r
 - types, 20
 - variable, 64
 - “X” and “Y” types, *see* capacitor, powerline rated
- CAPZero, 632
- CAS, 1023
- cascode, 102, 114, 115, 146, 148ff, 345, 369, 377, 502, 534, 544, 548, 549, 550
- folded, 149, 377, 498, 537
 - inverted, *see* cascode, folded
 - regulated (RGC), 551, 552
 - regulator, for HV, 693
 - series, for HV, 697
- catalogs, 1157
- cathode
 - ray tube (CRT), 1146
- CD audio, 904
- CDMA, 977
- CDR, 973
- ceramic resonator, 450, 1066
- cesium, *see* oscillator, atomic
- chain rule, 1104
- charge
 - integrator, *see also* AoE 2nd ed., pp 640–643
 - integrator (Coulomb counter), 935
 - MOSFET gate, 197g, 198s, 221r
 - pump, *see also* switchmode; capacitor, flying, 175n, 183, 638, 699r, 866
 - redistribution
 - ADC, 911, 952n
- charge injection
 - absence of, 841
 - in ADC, 913
 - in analog switch, 176t, 180, 181g, 300, 949, 950n
 - vs R_{ON} , 182g
 - in integrator, 920
 - in sample-and-hold, 256g
 - in switched-capacitor filter, 418
- choke, *see also* inductor, 29
 - common-mode, 585
- chopper, *see* op-amp
- cigar, *see* cigar
- circuit
 - BJT
 - basic, 91
 - breaker, 630
 - diagram
 - how to draw, 1105ff
 - integrated, *see* IC
 - linear, 14
 - loading, *see* loading
 - parallel, 2
 - RC
 - discharge waveform, 21g
 - Thévenin simplification, 23
 - resistor
 - shortcuts, 6
 - resonant, 52ff
 - series, 2

- parallel, 5
- resistor, 5
- clamp, *see also* SCR, 257
 - active, 257
 - active reset, in SMPS, 657
 - diode, 36
 - input transient, in SMPS, 669
 - op-amp, 914, 915
 - power supply, 692
- clearance, 663, 663
- clipping, 81
- clock
 - and data recovery (CDR), 973
 - feedthrough, 417
 - generation with PLL, 974
 - inputs and hysteresis, 808
 - real-time, 1064, 1087
 - recovery, 1040
 - skew, 757, 757, 759
- CMOS, *see* analog switch, *see* logic
- CMRR, 103, 388r, 515, 583
 - and source impedance, 365
 - at high-frequency, preserving, 359
 - differential amplifier, 376
 - ground-loop isolation, 583
 - instrumentation amplifier, 364, 364g, 367
 - vs frequency, 364
- coax, *see* cable
 - digital signals through, 1120ff
 - driving, 1120ff
- codec, 1144n
- coil
 - driver
 - precision, **899**, 900
- cold atoms, 365
- Coldfire, *see* microcontroller
- command bit, *see* computer, programmed IO
- command register, *see* computer, programmed IO
- common-mode, *see* amplifier, *see* comparator, *see* op-amp
 - pickup, *see also* CMRR, 583
 - torture test, 860s, 863s
- common-mode rejection ratio, *see* CMRR
- compact disc (CD), 995, 1135
- Compact Flash, 1064
- comparator, *see also* Schmitt trigger, 23, 129r, 236, 267, 289r, 700r, 812t, 813t, **809–817**, 878r, 1064, 1084
 - window discriminator, *see* AoE 2nd ed., p 669
 - antisaturation circuit, 812
 - cautions, 816
 - digital magnitude, 728, 728
 - driving logic from, 806ff
 - hysteresis
 - internal, 815
 - input
 - common-mode range, 812
 - input characteristics, **812ff**
 - input current, 814, 814g
 - input stage, 814
 - output current, 811, 811g
 - output stage, 811
 - output swing, 810
 - response time, 816g
 - saturation voltage, 811g
 - schematic, LM393, 270
 - speed, 815
 - supply voltage, 815
 - voltage
 - differential, 815
 - offset, 812
 - with hysteresis, 237
 - without hysteresis, 237
- compensation
 - active
 - of op-amp phase error, 314, 315g, 315t
 - dominant-pole, 282
 - of transimpedance amplifier (TIA), 537, **539ff**, 540–542g, 545
 - pole-zero, 284
- complex
 - conjugate, 1102
 - numbers, **1101**
 - plane, 1102
- compliance, *see also* current source, 8
- components
 - best avoided, 63p
 - confusing markings, 65p
 - itty-bitty, 65p, 269, 627p, 712n, 821n
 - passive, 56ff
 - through-hole, 65, 196, **268**, 269, 432n, 500, 601, 603, 617, 714, 715, 715p, 720, 769, 772, 782, 785, 786, 788, 789r
 - where to buy, 1154
- composite amplifier, *see* amplifier, composite
- compression, 1140
 - artifacts, 1141n
 - bitrate reduction, 1141
 - lossless, 1141
 - lossy, 1141

- computer, *see also* microcontroller, 1056
 architecture, 993–996
 Harvard, 994
 von Neumann, 994
 assembly language, 996, 1091
 BASIC, 1091
 block diagram, 994
 bus-oriented, 994
 C/C++, 1091
 CPU, 993
 data bus, 993, 995, 1032t, 1052r
 1-wire, 1038, 1039, 1085
 2-wire, 1064
 ADDRESS, 995, 1000
 ATA, 1030, 1065
 bidirectional, 1004
 bridge, 1093
 CAN bus, 1046, 1046ff, 1047, 1048, 1053r, 1064
 contention, 721
 control lines, 995
 DATA, 995, 1000
 differential, 1034n
 EISA, 1030n
 eSATA, 1031, 1040, 1053r
 Ethernet, 1048ff, 1053r, 1056, 1064
 Fastbus, 1030n
 FireWire, 1045, 1053r
 Firewire, 865n, 995, 1030
 Front Side, 993n
 Futurebus, 1030n
 GPIB, 1034, 1053r
 I²C, 1037, 1037ff, 1038, 1039, 1054r, 1056, 1064, 1099r
 I²C vs SPI, 1038
 IDE, 1030, 1053r, 1065
 ISA, 993n
 JTAG, 1039, 1039, 1054r
 MicroChannel, 1030n
 Multibus, 1030n
 multidrop, 1017, 1030
 NuBus, 1030n
 overview, 1030
 parallel, 1030, 1031, 1053r
 PATA, 1030, 1034, 1053r
 PC104/ISA, 995, 1015, 1030, 1047, 1052r
 PCI, 993n, 995, 1030, 1033, 1053r, 1056, 1064
 PCIe, 993n, 995, 1030, 1033, 1040, 1044, 1047, 1053r, 1056, 1064
 PCMCIA, 1047, 1056, 1064
 PLD address decoder, 1003
 point-to-point, 1030
 printer port (Centronics), 1034
 Q-bus, 1030n
 read cycle, *see* memory
 RS-232, 771, 804, 1030, 1054r
 SAS, 1030, 1031, 1040, 1053r
 SATA, 1030, 1034, 1040, 1044, 1053r, 1056, 1065
 SCSI, 1034
 serial, 1030, 1035–1049
 signals, 1016t, 1000–1016
 signals, summary of, 1015
 SPI, 1035, 1035ff, 1036, 1039, 1054r, 1056, 1064, 1099r
 SPI vs I²C, 1038
 STD bus, 1030n
 STROBE, 1000
 Unibus, 993n, 1030n
 USB, 865n, 995, 1030, 1045, 1045, 1047, 1053r, 1056, 1062, 1064, 1065
 VAX BI, 1030n
 write cycle, *see* memory
 direct memory access (DMA), 1013, 1053r
 flags, 993, 1052r
 IBM650, 1n
 instruction, 993
 instruction decoder, 993, 1052r
 instruction set, 1052r
 addressing modes, 997
 argument, 996
 jump, 999
 POP, 998
 PUSH, 998
 subroutine, 999, 1000
 x86, simplified, 997t, 996–1000
 interrupt, 1008–1013, 1053r
 acknowledgment, 1012
 autovectored, 1012
 handler, 1009, 1067, 1100r
 mask, 1013
 polling, 1011
 shared, 1011
 software, 1013
 interrupt hardware, 1009
 Java, 1092
 keyboard bus interface, 1005, 1006, 1008, 1009
 machine language, 996
 mass memory, 994
 memory, *see also* memory, 994, 1017–1030, 1054r, 1064

- cache, 994, 1052r
 - read cycle, 1020, 1022, 1024, 1025
 - SD, 1064
 - write cycle, 1020, 1022, 1024, 1025
- multidrop bus, 1017
- number storage in memory, 1051
- object code, 996, 999
- PC104, 1000p, 1016, 1017, 1018p
 - signals, summary of, 1015
- port, 995
- program
 - counter, 993, 1052r
 - example, 999
- programmed IO, **1001–1008**
 - command bit, 1053r
 - command register, 1007
 - data in, 1004
 - data out, 1001, 1002
 - read cycle, 1004, 1052r
 - status bit, 1005, 1053r
 - status register, 1005
 - write cycle, 1001, 1052r
- progress in, 993p
- pseudo-op, 999
- Python, 1092
- real-time IO, 995
- register, 993, 997, 1052r
- SBC, 1000p, 1016
- serial port, 1041
- software interrupt, 1013
- source code, 999
- stack, 998
 - pointer, 993, 998, 1052r
- subroutine, 999, 1000
- terminology, 992
- UART, *see* UART
- word, 993
- xy* vector display, 1002, 1002
 - block diagram, 1003
- conductance, **6**
- conduction
 - angle, 631, 633, 635
 - continuous mode, 637n, 642, 644ff
 - discontinuous mode, 637n, 642, 645, 666
- confusion central, 65p
- connector
 - audio, 62p
 - avoid these, 63p
 - banana, 61p
 - BNC, 56, 59, 62p
 - card-edge, 61
 - circular, 61p
 - DIN, 61p
 - DisplayPort, 1149
 - DVI, 1149
 - HDMI, 1148
 - Lemo, 61, 62p
 - MHV, 62p
 - microphone, 61p
 - Microtech EP-7S, 61p
 - miniDIN, 61p, 1148
 - MS, 61p
 - multipin, 61
 - phono, 63p
 - photographs of, 60–62p, 1148p
 - pin jack, 61p
 - RCA, 62p, 1147
 - rectangular, 60p
 - RF and shielded, 62p
 - RJ45, 1067
 - SC (fiber), 62p
 - shielded-cable, 59
 - SHV, 62p
 - SMA, 62p
 - SMB, 62p
 - ST (fiber), 62p, 871p
 - Supericon, 61p
 - TNC, 62p
 - type N, 62p
 - type-F, 63p
 - UHF, 62, 63p
 - video, **1147ff**, 1148p
 - XLR, 61, 62p, 348
- control
 - bang–bang, 608, 644n, 645, 645, 649, 650, 700r, 1073
 - proportional, 1073
- control loop
 - block diagram, 1072
 - PID, 1072
- converter, *see also* ADC; DAC; power, 30
 - AD/DA
 - errors, 882
 - linearity, **901**
 - performance parameters, 881–882, 987
 - power, *see* power supply, *see* switchmode, *see* voltage regulator
 - boost, *see also* switchmode, 30
 - buck, *see also* switchmode, 30
 - charge-pump, 183

- flying-capacitor, 183
 - time-to-amplitude, 916
 - V to f , 914
 - nonlinearity, 916g
- correlated double sampling, 553, 571n
- coulomb, *see also* charge, integrator, 2, 18
 - counter, 935
- counter, *see also* logic, 733
 - timing with, 465
- cow
 - spherical, 804
- cPLD, *see* programmable logic device (PLD)
- creepage, 663, 663, 664
- crest factor, 568, 983
- crossover
 - input, *see* op-amp
- crossover distortion, *see* distortion
- crosstalk, 581, 588
- crowbar, *see also* voltage regulator, 598
 - overvoltage, 598, 672, **690ff**, 691, 700r, 702r
- crystal, *see* oscillator, crystal
- CUPL, *see* programmable logic device (PLD)
- current, **1**, 68r
 - class-A, 754, 1076
 - comparator input, 814, 814g
 - comparator output, 811, 811g
 - conveyor, 99
 - critical, in SMPS, *see* switchmode
 - differential drive, 859
 - discontinuity
 - in switchmode converters, 649, 651
 - divider, 698
 - dynamic, 164, 186, 186, 793
 - of digital logic, 186, 186, 719
 - feedback, *see* feedback, current
 - gate leakage, 163
 - impact-ionization, 164
 - input
 - of digital logic, 795
 - of instrumentation amplifier, 362
 - of op-amp, 244
 - inrush, 637, 661, 668
 - Kirchhoff's current law, 2
 - limiting, 286, 597, 700r, 823, 824
 - foldback, 286, 693, 694, 694g, 823, 824, 824g
 - of outboard pass transistor, 695
 - load-sensing, 277
 - loop, 1041, 1087
 - mirror, *see* current mirror
 - mode, *see* switchmode
 - noise, *see* noise
 - probe, 1165
 - pulsation in SMPS, 650, 651
 - pulsation in switchmode converters, 649
 - quiescent
 - of logic families, 719
 - reactive, 41
 - ripple, 634, 635s
 - in boost converter, 647
 - in bridge converter, 659
 - in buck converter, 644
 - in storage capacitor, 634
 - in zener bias, 598
 - sensing, 278, 349, 350, 365, 754, 760
 - shoot-through, 186, 186, 660, 754, 760, 760g, 850, 944n
 - shunt, 277, 365, 946, 946
 - source, *see* current source
 - spy, 754, 754
 - steering, *see also* DAC
 - sawtooth generator, 919
 - suppression, 573
 - transfer ratio, 841, 1065
 - transformer, 946, 946
 - transient
 - output-stage, 850
- current mirror, **101ff**, 128r
 - active load, 105, 153, 496
 - compliance, 101, 104
 - Early effect in, 101
 - Wilson, 102, 102, 146, 546
- current source, 8, **85ff**, 431, **620ff**, 623g, 702r
 - 2-terminal, 622
 - 3-terminal regulator as, 620, 620, 621g
 - bandwidth of, 254
 - BJT, 85, 87, 91, 146, 534
 - compliance, 8, 27, 28, 86, 897
 - deficiencies of, 87
 - depletion-mode
 - FET as, 211, 622, 623g, 696
 - difference amplifier as, 350, 351
 - discrete, 622
 - floating, 897, 896–899
 - high voltage, 622, 696
 - high-voltage floating, 899
 - IC, 621, 622g
 - instrumentation amplifier as, 367
 - JFET, 142, 623g
 - JFET and BJT compared, 145
 - nanoamp

- programmable wide-compliance, 898
 - pulsed, 555
 - nanoamp wide-compliance, 896
 - noise of, **487ff**
 - op-amp, **228–230**, 242, 254, 344, 367, 622, 623, 897
 - Howland, 229, 230
 - oscillation in, 442
 - output resistance, 93n
 - precision, 351, 367, **899**, 900
 - resistor as, 85
 - slew rate of, 367
 - symbols, 9
 - transistor, *see* current source, BJT/JFET/depletion-mode
- curve tracer, 1119
- DAC, *see also* converter, AD/DA, 881, **883–902**, 1056, 1064, 1068, 1084, 1099r
- 1-bit, *see* delta-sigma
 - application examples, **893–901**, 987r
 - audio, 941t
 - charge redistribution, 906, 911, 911, 913
 - choosing, 893
 - code-change glitch, 894
 - current-steering, 885, **885–888**, 987r
 - generating voltage output from, 887, **887**
 - delta-sigma, *see* delta-sigma
 - exemplary, six, 888, 889, 891t
 - for DDS, 1068
 - for offset correction, 951
 - for zero correction, 951
 - frequency-to-voltage, 892, 987r
 - introduction, 881–883
 - multiplying, 413, **886**, 896t, 987r
 - PWM as, 890, 890, 892, 987r
 - PWM to, converter, 891
 - $R-2R$, **884**, 885, 987r
 - resistor string, **883**, 884, 987r
 - selected, 895t
 - switched-capacitor, 906, 911
 - tables, 891t, 895, 896t
 - types, 987r
- Darlington, *see* BJT
- photo, 839
- data bus, *see* bus, *see* computer
- data-acquisition system, *see* ADC, data-acquisition system (DAQ)
- datasheet
- too big, 1066n
- dB, 15ff, 68r, 351
- desert island, 15
- dB per octave, 51–52
- dB\$, 15n
- dBm, 15
- dc
- blocking capacitor, 43
 - power switching, 202
 - restoration, 37
 - supply splitter, 262
- dc-dc converter, *see* power supply, *see* switchmode
- DCE, 1041
- DDR, 1024
- DDR2, 1024
- DDR3, 1024
- DDR4, 1024
- DDS, *see* oscillator, DDS, 1069, 1070
- phase control, 1071
- debouncer, *see also* switch, 1067
- debugging
- microcontroller, in-circuit, 1096
- decibel, *see* dB
- decoder, *see* logic
- degeneration, *see* emitter, *see* source
- delay equalizer, 415
- delay line
- lumped element, 1130, 1132p, 1133
 - impedance of, 1131
 - transmission line, 1132p, 1134s
- delay time
- of filter, 400
- delta-sigma, 904, 989r
- 20-bit ADC, 936, 936
 - 24-bit ADC, 936, 938, 938, 939, 939
 - ADC, 937t, **924–943**
 - digital filter in, 926, 928
 - micropower, 943
 - application examples, **934ff**
 - audio ADC, 904n, 939t
 - block diagram, 926
 - charge integrator, 935
 - DAC, 890, **932**, 933, 940, 987r
 - demystifying, **925–932**
 - dynamic range, 927
 - vs OSR and m , 931g
 - ENOB, 930, 931g
 - even simpler, 934
 - fast multichannel IC, 957, 958
 - idle tones, 933, **934**, 934t
 - mitigating, 934

- simulation, 935g
 - “industrial” ADC, 938, 939
 - magic in the modulator, 929
 - microcontroller, implemented with, 934, 935
 - modulator, 926, 927
 - higher order, 930, 931
 - monotonicity, 933
 - noise shaping, 929g, **929ff**
 - powerline rejection, 955–957, 957g
 - pro-audio ADC, **938**, 942
 - pros and cons, **933ff**
 - simplest, 924
 - simulation, 931g, 932g, **930–932**
 - spectrum, 932g
 - suntan monitor, 924ff
 - the paradox, 926
 - time delay, 933
 - vs the competition, **940**
- DeMorgan’s theorem, 713
- derivative, 1103
- desensitivity, 117, 118
- design review, 1062
- Designs by the masters
 - instrumentation amplifier, 359
 - Keysight’s multislape converters, 921, 920–924
 - nanoamp programmable current source, 898
 - paralleling MOSFETs, 213, 214
 - powerline SMPS, 595p, 667s, 665–672
 - precision DMM, **342ff**
 - SR560 preamp, 512ff, 514
- desoldering station
 - favorite, 1156
- detector, *see* optoelectronics
 - proximity, 846
- device programmer, 769
- diac, 428
- diagram
 - ugly, 1106
- Dicke switch, 577
- dielectric
 - absorption, *see also* capacitor, **300**, 301g
 - constant, 18
 - isolation, 175
- differential, *see* amplifier
 - cable, **859–864**
 - logic signal, 705n
 - output, creating, 372, 373
 - pseudo, 583, 949
 - signal, 347ff
- differential amplifier
 - configurations, 376–378
- differentiation, 1103
- differentiator
 - bridged, 415
 - op-amp, 260
 - RC, 25, 26s, 51
- digital, *see also* logic
 - conquest over analog, history of, 703, 703n
 - filtering, 419
 - measurement, 140g
 - meets analog, **881–991**
 - multimeter, 10
 - potentiometer, 63, 184
 - signal processing (DSP), **418ff**
 - sampling, 419
 - television
 - broadcast, 1142
 - cable, 1142
 - satellite, 1143
 - spectrum, 1140s
 - vs analog, 703
- digital-to-analog, *see* DAC
- DIN
 - rail mount, 686
- diode, *see also* rectifier, 12, 31, **31ff**, 70r
 - AND gate, 711
 - as log converter, 37
 - catch, 642
 - clamp, 36
 - current-regulator, 143g, 623g
 - drop compensation, 35
 - fast recovery, 671
 - fault protection, 606, 607, 619
 - forward current, 294, 295g
 - forward drop, 31
 - freewheeling, 642
 - gate, 36
 - I vs V , 92
 - inductive clamp, 38
 - JFET as, 294
 - laser, *see* laser diode
 - LED, *see* optoelectronics
 - limiter, 37
 - MOSFET body, 199
 - operating point, 1116
 - photo, 537n, 539, 839, **839**, 871p
 - amplifier, 547, 548
 - wideband amplifier, 540
 - PIN, 871p
 - protection array, 805

- representative, 32t
- reverse recovery, 634, 635n, 670, 671
- Schottky, 32t, 35, 199n, 608, 634, 642, 643, 645–649, 651, 655, 657, 665, 666, 671, 696, 717, 757, 792, 914, 915
- suppression, 75
- tunnel, 7, 1117
- varactor, 64, 435, 440, 441, 962, 971, 973
 - capacitance vs voltage, 441g
- zener, *see also* voltage reference, 12ff, 82, 199, 670, 674, 696–698, 701
 - as voltage regulator, 595
 - biasing, **675**
 - buried, 546
 - drift, 675
 - dynamic resistance, 675g
 - dynamic resistance of, 13
 - for crowbar, 690
 - IC, **676ff**
 - low voltage, 13g
 - noise, 676n
 - tempco, 675g
 - the astonishing LTZ1000, 675
- DIP (dual in-line package), *see* IC, packages
- direct digital synthesis, *see* oscillator, DDS
- direct memory access, *see* computer
- discharge
 - curves, of battery, 687g
 - of high-voltage supply, 211
 - RC, 21
- discontinued parts, 273 (box)
- display
 - LCD
 - interface timing, 1031
 - xy vector
 - interface, 1002, 1002
- display devices, *see* optoelectronics
- DisplayPort, *see* connector
- distortion, *see also* op-amp, distortion, 309
 - barn-roof, 95, 95s
 - crossover, 286, 309, 311
 - effect of feedback, 235s
 - in push-pull follower, 107
 - of differential amplifier, 386, 386g
 - of filtered sinewave, 436
 - of modified sinewave, 674
 - of op-amp, **329ff**, 331, 332g
 - rail-to-rail, 318
 - of phase-shift oscillator, 439
 - of photoconductive cell, 437
 - of switched-capacitor sinewave, 436
 - of Wien-bridge oscillator, 437, 438
 - test circuit, 332
 - ultra-low, oscillator, 437
- dithering, 971
- divider
 - voltage, **7**
- DMM, 10
 - Agilent's accurate, **342ff**
 - block diagram, 343
 - current sink, 344
 - front end, 343, 344
 - gain block, 345
 - ranging, 345
 - favorites, 1156
- Dobkin, Bob, 604 (box), 679
- dogs, 63p
- dominant pole
 - compensation, 282
- double buffering, 1003
- doughnut, 29
- DPCP, 1149
- DRAM, *see* memory, dynamic; computer
- DSL, 1145
- DTE, 1041
- dual-slope
 - conversion, *see* ADC
- dual-tracking, *see* voltage regulator
- duty cycle, 643
- duty-cycle
 - limiting, 465
- DVD, 703n, 847, 995, 1139
- DVI, *see also* connector, 1065
- dynamic range
 - of delta-sigma converter, 927
 - of switched-capacitor filters, 418
 - vs precision, 292
- Early effect, **92**, 93n, 99, 99n, 101g, 127r, 151n
 - configurations that avoid, 102, 127r, 148
 - in current mirror, 101
- Early voltage, *see* voltage, Early
- Ebers-Moll model, **90ff**
- Eden
 - garden of, 549
- edge
 - detector, 26
 - leading, 25
 - trailing, 25
- EEPOT, *see also* potentiometer, 63, 1070

- egg
 Easter, *see* if you can find all eight
- electrical engineer
 view of biology, 805
- electrical tape, 63p
- electromagnetic interference, *see* EMI
- electrometer, 10n, 297, 570ff
- electromotive force, *see* EMF
- electrostatic discharge, *see* ESD
- EMF, 2
 back, 28
- EMI, 649, 668
 in instrumentation amplifiers, 365
- emitter, *see* optoelectronics
 degeneration, 88, 96, 98, 116, 126r, 128, 129r, 308, 502
- emitter follower, *see also* BJT, 79, 79–85, 91
 as voltage regulator, 82
 biasing, 83
 cancelling offset, 85, 87
 current flow in, 81
 example, 84
 impedances of, 80
 JFET current-sink pulldown, 144
 noise of, **487ff**
 output impedance of, 94
 revisited (Ebers-Moll), 93
 with split supplies, 84
- e_n , *see* noise, density, voltage
- e_n -C, *see* transimpedance amplifier
- encoder
 rotary, 1069
- energy
 density
 battery vs capacitor, 690g
 in capacitor, 19
 in inductor, 28
 storage
 battery vs capacitor, 690t
- ENOB (effective number of bits), 902, 907t, 930, 931g, 987r
- equalization, 380, 381, 858, 864, 864, 865s, 867g
- equivalent series inductance, *see* capacitor; resistor
- equivalent series resistance, *see* capacitor
- error
 budget, 293, 295–299, 307, 388r
 component, 299, 388r
- eSATA, *see* computer, data bus
- ESD, *see also* human body model; spike, 200, 200t, 804
 input protection, 258, 362
- ESL, *see* capacitor; resistor
- ESR, *see* capacitor
- Ethernet, *see also* computer, data bus, 862, 995, 1030, 1044, **1048ff**, 1064, 1067, 1084, 1093, 1099r
 3-level signaling in, 1043n, 1049
 4b/5b coding in, 1043n, 1049
 8b/10b coding in, 1044, 1049
 Manchester coding in, 1043
 power over (PoE), 1049n
- Euler, Leonhard, 1102
- eye diagram, 864, 864, 865, 866s, 977, 991r, 1030, 1031s
- fan, *see also* AoE 2nd ed., p 858, 627
- farad, 18
- feature size
 scaling, 793n
- feedback, **115ff**, 130r, **223ff**
 BJT examples, 121
 Blackman's impedance relation, 120
 closed-loop gain, 117
 compensation, 120
 current, 527
 effect on amplifier circuits, **117ff**
 effect on input impedance, 118
 effect on output impedance, 119
 gain equation, 116
 improved frequency response, 118
 in PLL, 962, 963
 loading by the feedback network, 120
 nonlinear, 276
 nonlinear control, 1078
 output-current sensing, 120
 PID, 1072, 1072, 1077, 1080
 circuit, 1078
 convergence, 1079g
 tuning, 1072, 1077
 predictability of gain, 117
 series, 118
 shunt, 119
 split, 263, 286, 915
 stability, 120
 in switchmode converters, 650
 with inductive load, 901
- ferrite, 655, 669–672, 696–698
- FET, *see also* JFET, MOSFET, 115, **131ff**
 analog switch, *see* analog switch
 basic circuits, 140
 depletion-mode
 as current source, 622

- dynamic gate current, 164
- enhancement and depletion, 135, 219r
- family tree, 134, 136
- gate current, **163**, 220r
- gate drive, 137
- gate leakage current, 163
- G_{\max} , 141t
- interdigitation, 140
- JFET and MOSFET, 134
- leakage
 - circuit cure for, 259
- linear region, 137, 137g, 220r
- linear switch, *see* analog switch
- manufacturing spread, 140g, 138–140, 145g, 157, 158, 169, 169g
- matching, 139
- operating regions, 219r
- polarities, 131, 219r
- polarity, 136
- probe, 810p
- quadratic region, 132, 137, 137g, 138, 147, **165ff**
- resistive region, 132
- saturation current, I_{DSS} , 136, 139g, 361
- saturation region, 132, 137g, **137**, 147, **165ff**, 219r
- similarity to BJT, 132
- square law, 137ff, 165
- subthreshold region, 138, 139g, 166, 167g, 168, 220r
- switch, 132, **171**, 220r
- tempco of I_D , 138g, 138n
- terminal nomenclature, 131
- threshold voltage (V_{th}), 136n, 137ff, 137, 138g, 147
- transconductance (g_m), 132, 141t, **146**, 219r
- transfer characteristics, 135g, 137g, 139g, 142g
- types, 134
- $V-I$ curves, 132, 133g
- V_{GS} spread, 140g
- FEXT (far-end crosstalk), 581
- fiber optics, **847ff**, 875p, 879r
 - integrated transceiver, 850, 850, 875p
 - ST/SC, 849, 875p
 - TOSLINK (EIAJ), 847, 848s, 875, 875p
 - Versatile Link, 849, 875p
- field-effect transistor, *see* FET
- filter
 - RC highpass, 69r
 - RC lowpass, 69r
 - active, **396–399**, **405–415**, 423r
 - bandpass, 411ff
 - lowpass, 241, 400ff
 - Sallen and Key, 242g
 - universal, 416, 417, 417, 418
 - allpass, 415
 - analog FIR, 985
 - anti-alias, 395, 903ff
 - attenuation
 - degraded by ESR, 393g
 - bandpass
 - noise bandwidth, 564t, 565g
 - Bessel, 402g, 403, 409g, 423r
 - VCVS, 408
 - biquad, 411, 423r
 - brickwall, 391g, 477, 904
 - equivalent bandwidth, 477, 561, **561**, **563ff**
 - bridged differentiator, 415
 - Butterworth, 401, 401, 402g, 409g, 423r, 904
 - LC, **1113ff**, 1114t
 - VCVS, 408
 - Cauer, 402
 - characteristics, 400, 401g, 423r
 - Chebyshev, 401, 402g, 409g, 423r
 - phase and amplitude, 400g
 - VCVS, 408
 - vs RC, 396g
 - comparison, 402g
 - continuous-time, 397, 406, 423r
 - delay equalizer, 415
 - delay time, 400
 - digital, 419ff, 424r
 - in delta-sigma, 926, 928
 - of PRBS, 981
 - response, 421g
 - discrete-time, 418, 423r
 - eco-friendly, 1076
 - effect of component tolerances, 402g
 - effect of non-ideal capacitors, 392
 - electrically tunable, 412
 - elliptic, 402, 403g, 1071
 - equiripple, 401, 402
 - finite-impulse-response (FIR), 419, 421g, 424r
 - frequency response
 - comparison, 409g
 - frequency-domain characteristics, 399
 - Gaussian, 404
 - highpass
 - approximate, 43
 - exact, 48
 - VCVS, 408
 - implementation, **405–418**, 423r
 - inductorless, *see* filter, active

- infinite-impulse-response (IIR), 419, 424r
- LC, 54g, 54p, 55s, 393, 423r
 - brickwall bandwidth, 561
 - multisection, 394
- linear-phase, 400, 404
- linearity, 422
- lowpass
 - after transimpedance amplifier, 542
 - anti-alias, 395
 - approximate, 42
 - dc-accurate, 418
 - exact, 50
 - FIR, 420
 - IIR, 420
 - in switching amplifier, 109, 673
 - of PRBS, 981
 - VCVS, 407
- maximally flat, 401
- multiple-feedback, 413
 - effect of op-amp Z_{out} , 414g
- node of difference amplifier, 355
- noise bandwidth, 564t, 565g
- notch, 414, 423r
- overshoot, 400
- passive, **391–396**, 423r
- performance parameters, 399
- phase shift, 404g
- phase-sequence, 455, 456, 456g
- power-supply, 32, 699r
- powerline, 631
- RC highpass
 - approximate, 43
 - exact, 48
- RC lowpass
 - approximate, 42g
 - exact, 50
 - phase shift of, 50g
 - phasor diagram, 51
 - switchable, 182
- RC, 402g, 423r
 - brickwall bandwidth, 561
 - loading by, 44
 - phase shift, 393g
 - response, 392g
 - worst-case impedance of, 44
- recursive, 419
- ringing, 400
- ripple, 399
- rise time, 400
- Sallen and Key, 399, 409, 423r
- settling time, 400
- skirt, 399
- specifying, 403g
- state-variable, 410ff, 423r
 - bandpass, 411
- step response, 405g, 406t
 - comparison, 405g, 406t
- switched-capacitor, 397, 406, **415ff**, 423, 424r, 436
 - advantages, 416
 - configurations, 417
 - drawbacks, 417
 - noise, 418g
 - sine from square, 436, 436s
- Thomson, 403
- time delay, 404g
- time-domain characteristics, 400
- tracking, 436, 577
- twin-T, 414, 423r
- types, 400ff
- VCVS, 407, 408, 408t, **407–410**, 423r
 - effect of op-amp Z_{out} , 414g
 - highpass, 408
- finite state machine (FSM), *see* logic
- FIR, *see* filter, digital
- FireWire, *see* computer, data bus
- firmware, 1059
- first-in, first-out, *see* logic
- flash
 - conversion, *see* ADC
 - memory, *see* memory
- flicker, *see also* noise, 1/f
 - of ADC code, 937
- flip-flop, *see* logic
- flowchart, 1059
- flyback, *see* switchmode
- flying
 - amplifier, 367
 - capacitor, *see* capacitor, flying
- foldback, *see* power supply; voltage regulator
- follower, *see* emitter follower, source follower, op-amp
- forgettory, 994
- forward
 - converter, *see* switchmode
- Fourier transform, 395n
- FPGA, 788, 789r, 1034, 1039, 1056n, 1063, 1094p, 1097, 1100
- frequency
 - analysis of reactive circuits, **41ff**
 - angular, 14
 - beat, 975, 976

- compensation, **280ff**
 - in linear regulator, 597
- dithering, 649n, 971
- intermediate (IF), 562, 1143
- log sweep, 1072
- modulation, *see* modulation
- multiplier, 963, 964
- shifting, 395
- spurs, 968, 969, 973, 1069, 1070
- synthesis, 394, 451, 471r, **968–971**
- synthesizer, 17, 1085
 - microcontroller, **1068–1072**
- to voltage converter, 892
- translation, 562
- f_T , *see* op-amp, gain vs frequency
- full duplex, 1036, 1045, 1054
- function generator, 17
 - arbitrary, 18
 - favorites, 1156
- fuse, 630, 699r
 - rating, 631
- GAL, *see* programmable logic device (PLD)
- galvanic isolation, 840, 866
 - CAN bus, 1048
- Garwin, R. L., 571n
- gate
 - delay
 - vs power, 792g
 - vs voltage, 794g
 - input current, 795g
 - logic
 - as pulse generator, 459
 - CMOS, 185
 - speed
 - vs power, 719g, 792g
 - vs voltage, 719g, 794g
 - universal, 715, 717
- GBW, *see* BJT, gain-bandwidth product, *see* op-amp, gain vs frequency
- generalized impedance converter, 398
 - op-amp bandwidth, effect on, 399g
- Gilbert cell, 162
- glitch, *see also* logic, 738
 - code-change, in DAC, 894
- GLONASS, 451n
- glossary, 1170
- GPIB, *see* computer, data bus
- GPIO, 1087
- GPS, 451, 1056, 1064
- Gray code, **708**
 - binary conversion, 711
- ground, 2
 - bounce, 758s, 759, 793, 850, 851, 879r
 - inductance, 758
 - loop, 442, 582
 - isolation, 349, 350
 - noise, 850, 851
 - oscilloscope probe, 1165
 - plane, 581, 758, 759
 - separate analog and digital, 917
- grounded coplanar waveguide, 1121
- grounding, 579ff, **582ff**, 593r, 758
 - between instruments, 583
 - blunders, 582
- group delay, 400
- guard, 358, 360, 587
- Gummel plot, 92g, 127r, 500
- Gummel-Poon, 93n
- gyrator, 397ff
- H-bridge, 655, 659, 891, 1087
- half duplex, 1037, 1045, 1087, 1087n
- Hamming, *see* window, sampling, 977
- Hanning, *see* window, sampling
- hard disk (hdd), 1139
- HDCCP, 1149
- HDL, *see* programmable logic device (PLD)
- HDMI, *see also* connector, 1044
- HDTV, 1141
- heat, **623ff**, 701r
- heatsink, **623ff**, 625p, 701r
 - air flow, 627
 - insulating, 626
 - LED, 833p, 870
 - PCB foil as, 626, 627g
 - sizing, 626g
 - sizzle test, 625
 - thermal resistance of, 626g
- heel
 - Achilles', 536n
- henry, *see* inductor
- heterodyne, 563
- heterodyne, 562
- Hewlett, William, 437n
- hex file, 1062
- hexadecimal, *see* number, *see* number
- high voltage
 - clearance distance, 663
 - creepage distance, 663, 664, 665p

- pulse generator, 333, 919, 920
 - hour of power, 466, 467
 - hour of power (design example), 466
 - human
 - body model (HBM), 200, 804ff, 805, 866, 877r
 - system interface (HI), 1062, 1100r
 - humidity
 - and MOSFET damage, 200
 - effect on ICs, 684
 - hybrid
 - signal isolator, 1049
 - hysteresis, *see also* Schmitt trigger, 237
 - clock inputs, 808
 - in tunnel diode, 1118
 - thermal, 683
 - hysteretic
 - SMPS, *see* switchmode
 - I²C, 889, 1031, 1033, 1064, 1084, 1093, 1098
 - in DAQ, 956
 - microcontroller peripherals, 1089, **1087–1090**
 - I²C, *see also* computer, data bus
 - bridge, 1087
 - I²C
 - address selection, 954, 955
 - IC
 - discontinued, 273 (box)
 - packages
 - DIP, 3p, 57p, 65p, 73p, 224p, 225, 269, 340, 443p, 664, 715p, 758, 765p, 855, 1062
 - SMT, 73p, 224p, 225, 269, 340, 443p, 715p, 758, 765p, 855
 - parallel interface, *see also* computer, data bus, 1031, 1033
 - example, 1031, 1033
 - serial interface, *see also* computer, data bus, **1035–1049**
 - IEC power entry, 629
 - IEEE 1394 (FireWire), *see* computer, data bus
 - IGBT (insulated-gate bipolar transistor), 207, 222r, 695
 - desaturation, 843
 - immediate argument, 996
 - impedance, **40ff**, 68r
 - audio, 351
 - characteristic, of transmission line, 1120
 - converter, generalized (GIC), 398
 - op-amp bandwidth, effect on, 399g
 - converter, negative (NIC), 397
 - in parallel, 46
 - in series, 46
 - input
 - of difference amplifier, 352, 354
 - of differential amplifier, 376
 - of op-amp, 245
 - matching, 1124
 - of LC, 52, 444n
 - of RC, 49g
 - of common-emitter amplifier, 88
 - of emitter follower, 80
 - of sources and loads, 79
 - of transmission line, 1124
 - output
 - of op-amp, 309
 - of RRO op-amp, 316
 - output, of op-amp, 246
 - small-signal, 81
 - transmission-line matching, 1126
- i_n , *see* noise, density, current
- in-phase, 395n
- inductance
 - leakage, 30, 633–635, 656, 659, 667, 668
 - disadvantages, 633n
 - energy in, 669
 - in powerline transformer, 633
 - magnetizing, 30, 656, 666, 667, 669
 - of coil, 28
 - of op-amp output, 250g
 - sensor, 1087
- inductive
 - kick, *see also* spike, 38
 - loads, 38
- inductor, **28ff**, 29p, 68r
 - A_L value, 670
 - drawbacks of, 396
 - flyback, transformer as, 655, 656
 - international notation, 5n
 - reactance of, 44, **45**, 49g
 - some magic with, 29
 - stored energy, 689, 700r
 - in switchmode converter, 636, 655, 666
 - variable, 64
 - volt-second balance, 30, 643
- input
 - protection, 175, 175, 210, 294, 362, 805, 948, 951
 - logic, 804, **804**
 - robust, 362
- inrush current, *see* current, inrush
- instrumentation amplifier, 273, 288r, 297, 306, 363t, 390r, 512, 1073, 1074
 - as current source, 367

- autozero, 342, 370
- bootstrapped power supply, 359, 359
- classic, 357
- CMRR, 347, 358, 363t, 364, 364g, 367
 - vs frequency, 364
- CMRR depends on gain, 358
- CMRR vs R_{source} mismatch, 366g
- common-mode range, 367, 1074
- configurations, 357, 368, 368ff, 369
- discrete, 361
- EMI, 365
- hybrid, 513
- in DAQ, 950
- input current, 362
- JFET-input, 512
- miscellany, 362
- noise, 362
- noise depends on gain, 358
- offset drift, 306
- offset trim, 366, 366
- offset voltage, 306
- PGA, **370**, 370, 371t
- resistor matching, 358
- roll-your-own, 359
- signal guards, 358
- integrated circuit, *see* IC
- integrating
 - conversion, *see* ADC
- integrator
 - droop, 257–260
 - in active filter, 406
 - in PLL, 962
 - in quadrature oscillator, 453
 - op-amp, 230, 231s, 257–260
 - RC, 26, 51
 - switched-capacitor, 416
- interdigitation, 140, 515
- interference, 478, 579ff
 - intersymbol, 864
- interlace, 1137n
- Internet
 - video streaming, 1144
- interrupt, *see* computer
- inverter
 - ac power converting, 673, 673s
 - charge-pump, 183
 - flying-capacitor, 183
 - logic
 - CMOS, 185
 - nMOS, 185
 - op-amp, 225
 - optional, 232
 - pMOS, 185
- inverting
 - switchmode converter, *see* switchmode
- IP, *see* programmable logic device (PLD)
- ISA, *see* computer, data bus
- isolation
 - barrier in offline SMPS, 663
- jetpack, 1099r
- JFET (junction field-effect transistor)
 - bootstrapped drain, 343, 344
- JFET (junction field-effect transistor), *see also* FET,
 - 134, 217t
- 1/f noise, 510, 517g
- amplifier
 - biasing, 220r
 - common-source, 149
 - g_{os} gain error, 167
 - instrumentation, 512, 513
 - low noise, 346, **509–520**
 - maximum gain G_{max} , 166
 - with cascode, 148
- as diode, 294
- as variable resistor, **161ff**, 437, 438
 - linearizing, 161, 162, 162g
- biasing, 150, 150n, 156, 513
- capacitance, 170, 510, 519
- care and feeding of, 346
- characteristic curves, 143g
- current noise, 511g, **511**
- current source, 142, 623g
 - as BJT follower pull-down, 144
 - self-biased, 143g, 145g
- deep subthreshold region, 166, 167g
- differential amplifier, 152, 343, 512, 513
- dual, 139, 515
- dynamic gate current, 164
- gate current, 163g
 - impact ionization, 164g, 546
- G_{max} , 141t
- hybrid amplifier, 151, 153g, 155g, 343, 344, 512, 513, 544
 - compensation, 154, 154g
 - vs FET op-amp, 155
- impact-ionization current, 164
- in Wien bridge oscillator, 437, 438
- leakage, *see* JFET gate current
- linear circuits, **142ff**

- low distortion, 346
- low noise
 - hybrid op-amp, 534
- low-noise, 516t
 - selecting, **515**
- mini-table, 141t
- noise, 346, 500, **509–520**, 591r, 593r
 - reduction by paralleling, 509
 - vs BJT, 517
- op-amp
 - fast, 155t
- operating point, 156, 1116
- oscillator, 155, 441
 - in PLL, 395
 - spectrum, 442g
- output conductance, 148n, 166
- output resistance, 148n, 166, 517
- pinch-off reference, 680, **680**
- pinch-off voltage tester, 240
- pinch-off voltage, V_p , 136
- schematic symbols, 135
- series-feedback pair, 150, 151g
- source follower, *see* source follower
- subthreshold region, 166g, 167g, 168g, **166–170**
- switch, 220r
- threshold voltage (V_{th}), 137, 147, 166, 167g, 169g
- transconductance, 132, 141t, **146**
 - vs drain current, 168g, 169, 169g
 - vs drain voltage, 170, 517
 - within a family, 169, 169g
- transfer characteristics, 135g, 137g, 139g, 142g, **165ff**, 166–169g
- trimming offset with DAC, 345
- V_{GS} spread, 140g
- voltage noise, 346, **509–511**, 518–520g
 - theory vs measurement, 509g
 - vs frequency, 510g
 - vs transconductance, 509g
- voltage reference, 680, **680**
- vs MOSFET, 170g
- jitter, 427, 457g, **457**, 464, 864, 909, 966, 968, 973
 - rejection in PLL, 976
- Johnson noise, **474ff**, 475g, 475t, 482g, 494g, 526g, 569, 590r
 - as noise source, 557
 - calculation example, 486
 - gain resistor contribution, 152, 352, 358, 379, 384, 908
 - greater at low gain, 387
 - in differential amplifier, 520
 - in JFET channel, **509**
 - in TIA feedback resistor, **537ff**
 - eliminating, 552
- joule, 2
- joy
 - and pain, 65
- JTAG, *see also* computer, data bus, 764, 769, 787r, 1031, 1039, 1064
 - bootloader, 1095
- jump, 999
- Karnaugh map, *see* logic
- KCL, KVL, *see* Kirchhoff's laws
- Kelvin connection, 277, 294n, 350, 1073
- keyboard, 1067
 - parallel bus interface, 1006, 1008
- keypad, 1084
 - hex, 1071, 1072
- Kirchhoff's laws, 2, 68r, 1111
- L network, 1127
- ladder
 - $R-2R$, 234
 - DAC, 884, 885
 - replaced by charge redistribution, 911
- lamp, 62, 437
 - as a problem load, 694
 - neon, 428
- Lantronix XPort, 1067
- Larkin, John, 360
- laser diode, 830p, 833, 834s, 975, 975
 - current, 834s
 - driver, 834, 834n
 - linearizing, 834s
 - modulating, 835
- laser trimming, 244, 305, 352, 357, 416
- latch, *see* logic
- latchup
 - in analog switch, 174
- LC, *see also* filter, LC, 52
 - Butterworth filter, **1113ff**, 1114t
 - damped oscillation, 53g
 - filter, 54g, 54p, 55s
 - filter examples, **1113ff**
 - impedance of, 52, 444n
 - notch, 53
 - oscillator, *see* oscillator, LC
 - parallel, 52
 - resonant circuit, 52, 69r
 - series, 52

- tank, 53
- trap, 441n
- LC
 - series, 394
- LCD, *see* optoelectronics
- LDO, *see* voltage regulator, low-dropout
- leakage, *see also* capacitor; JFET, 420, 1065
 - spectral, 420
- leap year, 969n
- Lebowski, *see* egg
- LED, 13, 62, 575, 830p, **829–833**, 878r
 - angular illumination, 830, 831g
 - arrays, 831
 - as bias reference, 86n
 - backlight, 1087
 - BJT driver, 76
 - constant-current drive, 831
 - current-source drive, 622
 - desk lamp, 833p, 870
 - driver, 1090
 - driver ICs, 832t
 - driving
 - series string, 831
 - driving from comparator, 13, 14
 - driving from logic, 817ff, 832
 - driving from MOSFET, 206, 465, 466
 - driving from TTL, 718n
 - forward drop, 76g, 827g
 - high-current driver, 834s
 - lamp (design example), 832
 - multiplexed display, 751, 751–752
 - multiplexed drive, 744n
 - organic, *see* OLED
 - panel-mount, 870t
 - pulsed, 466, 834s
 - synchronous detection of, 577
 - voltage budget, 752
 - wavelength, 76
- Lehrer, Tom, 1103
- LFSR, 558, 771
- lighting, *see also* optoelectronics; LED
 - theater, 1084
- lightning detector (design example), 497
- limiter
 - diode, 37
- line driver
 - difference amplifier, 351
- linear
 - circuit, 14, 68r
- linearity
 - converter, 882, 901
 - DNL warning, 902
 - INL vs DNL, 901, 901
- linearizing
 - JFET resistor, 162
 - optocoupler, 844
 - via lookup table, 1070, 1100r
- Little Logic, *see* mini-logic
- LMOS, *see* mini-logic
- LO, *see* oscillator, local
- load
 - active, 105, 158
 - capacitive
 - logic, 851, 851
 - op-amp, 263s, 264, 264
 - dump, 618
 - inductive, 38
- load lines, 145g, 156, 156g, **1116ff**
- loading, 10ff, 11g, 69r, 79
- lock-in, *see* bandwidth, narrowing
- lockup, *see* logic, pathology
- logarithmic
 - frequency sweep, 1072
- logic
 - 0 and 1, 704
 - 1-of-8 decoder, 727
 - 4-bit full adder, 728
 - Verilog code for, 729
 - 5V-tolerant, 798
 - 8-input multiplexer, 726
 - active-HIGH, active-LOW, 714
 - adder, 728
 - arithmetic logic unit (ALU), 728, 993, 1052r
 - assertion-level, 713
 - asynchronous, 733, 734, 734s, 743s
 - BiCMOS, 714, 717n
 - buffer, *see* buffer, logic
 - capacitive load, 851, 851
 - class-A current, 186, 186, 754
 - clock
 - global, 777
 - clock skew, 757, 757, 759, 801
 - CML, 868
 - CMOS, 221r, 714, 790–794
 - characteristics, **718ff**
 - circuits, 791
 - failure modes, 760
 - input current, 795g
 - minimizing power, 754
 - open inputs with, 759, 760

- output current, 798g
- output voltage, 797g
- pathology, 759
- shoot-through current, 760, 760g
- speed vs power, 792g
- speed vs voltage, 794g
- threshold skew, 760
- threshold voltage, 797g
- transfer characteristics, 796g
- weak outputs, 827
- combinational, **708–728**, 762r
- combinatorial, 708
- contention, 721, 722, 730
- counter, 742t, **741–744**, 762r
 - asynchronous, 733, 734, 734s
 - modulo-*n*, 748ff, 750
 - modulo-*n*, timing, 750g
 - ripple, 733, 734, 734s
 - synchronous, 737, 737s
- current
 - class-A, 754, 760, 760g
- D-register
 - Verilog code for, 741
- data bus, 720, 721
- DCL, 790
- decoder, 726
 - expansion, 727
 - Verilog code for, 727
- delay
 - vs power, 792g
 - vs voltage, 794g
- demultiplexer, 726
- digital vs analog, 703
- diode, 711
- divide-by-2, 731, 732
- divide-by-3, 734, 743, 743s
 - asynchronous glitch, 743s
 - synchronous, 735
 - Verilog code for, 736
- driving
 - external loads, 721, 818, **817–829**, 877r
 - from comparator, 806
 - from op-amp, 808
 - pre-emphasis, 858
- driving ac loads from, 821, 822
- driving negative loads from, 821, 822
- DTL, 790
- dynamic current, 186
- ECL, 714, 717n, 718, 718, 722, 750, 790
- edge rate, 801, 801s
- enable, 720, 752
- excluded states, 735
- expansion, 726, 726, 727
- families, 704n, 706t, 714, **717ff**, 763r
 - characteristics, **718ff**
 - choosing, 719, 794, 877r
 - chronology, 790–794
 - circuits, 791
 - CMOS, 790–794
 - DTL, 790
 - ECL, 790
 - input, 718, **795**, 797g, 877r
 - input current, 795, 795g
 - interconnecting, 799, **798–802**, 877r
 - life cycle, 715g
 - logic levels, 706 (box), 718
 - output, 718, 796, 797, 798g, 877r
 - RTL, 790
 - speed and power, 719
 - speed vs power, 719g, 792g
 - speed vs voltage, 719g, 794g
 - supply voltage, 718
 - threshold voltage, 796, 797g
 - transfer characteristics, 796g
 - TTL, 790–793
- fan-out, 711, **794ff**, 795n
 - none in transmission gate, 725, 726
- FIFO, 747
- flip-flop, 196, **728ff**, 762r
 - clocked, 730, 732
 - debouncer, 802, 802s
 - edge-triggered, **731**
 - hold time, 732
 - master-slave, 732
 - propagation time, 732
 - RS*, 729
 - setup time, 732
 - setup time violation, 733g, 733s
 - toggling, 731, 732
 - type-*D*, **731**, 732
 - type-*JK*, 731
 - type-*T*, 731
- gate, *see also* buffer, logic; Single Gate, **708–724**, 762r
 - 2-input select, 724, 725
 - AND, 709, **709**
 - circuits, discrete, 711
 - example, 712, 714
 - exclusive-OR, 710
 - interchangeability, 713

- inverter, 709, 710
- NAND, *see also* memory, nonvolatile, 186, 710, 710, 1027
- NOR, *see also* memory, nonvolatile, 710, 710, 1027
- NOT, 709, 710
- OR, 709, **709**
- standard, 709
- transmission, 172, 725, **725**
- universal, 715, 717, 800
- XOR, 710, 710, 737, 753, 771, 782, 959, 977, 984
- XOR realization, 722
- glitch, 738, 739, 743s
- glue, 793
- GTL, 852
- hardware description language, *see also* programmable logic device, *see* logic, HDL, 711
- HDL, *see also* programmable logic device, 711
- HIGH and LOW, 704
- hold time, 732
- IC packages, 715p
- identities, 722t
- input characteristics, **795**
- input overdrive, 806
- input protection, 804, **804**
- inputs, 795
 - current, 795, 795g
 - driving, **802**
 - overcurrent, 806
 - pulldown, 805
 - pullup, 805
 - unused, 806
 - voltage, 797g
- interfacing, **790–868**
 - between logic families, 799, **798–802**
- isolator, 823
- jam-load, 748
- Karnaugh map, 723
- keeper circuit, 802, 803
- latch, 740
- level translator, 800, 802
- levels, 17, 706 (box), 762r
 - CAN bus, 1047
 - symmetrizing, 980
- life cycle, 715g
- lockup, 755
- LVDS, 794
- LVPECL, *see* LVPECL, 794
- magnitude comparator, 728, 728
- metastability, **732**, 733g, 733s, 756
- Mickey-Mouse, 468
- micropower design, 753
- mini, 712n, 715n, 793
- minimization, 723
- MOSFET, 184
- multiplexed display, 751, 751ff
- multiplexer, 724
 - expansion, 726, 726
 - race condition in, 756, 756
 - Verilog code for, 726
- multiplier-accumulator, 728
- NECL, 718, 718n
- negative-true, 704n, 714
- nMOS, 712
 - driving LED, 827g, 828
 - driving loads, 828
 - input characteristics, 828
 - interfacing, 826ff
 - output characteristics, 827
 - output circuit, 827
- open-collector, 721, 800, 807, 811, 817, 996
 - as level translator, 721
- open-drain, 721, 721, 800, 807, 811
- output characteristics, **796**
 - voltage vs current, 798g
- parity generator, 728
- pathology, **755–760**, 763r
 - unspecified rules, 757
- PECL, *see also* PECL, 718, 718n
- positive-true, 704n, 714
- power
 - dynamic, 754
 - minimizing, 754
- preload
 - asynchronous, 748, 752
 - synchronous, 748
- priority encoder, 727
- probing, 808, 809s, 810p
- programmable, *see* programmable logic device
- propagation time, 710s, 732
- pulse generator
 - design example, 739
 - with flip-flops and counters, 739
- quiet, 759, 793
- race, *see also* runt pulse, 724n, 738, 748, 756
- register, *see also* computer, 740, 762r, 993
 - power, 819, 819t
 - shift, 744, **744**
- removal time, 758

- reset
 - asynchronous, 743
 - synchronous, 743
- reset/supervisor, 756t
- ringback, 759n
- robust link, 1124
- RTL, 711n, 712, 790
- runt pulse, *see* runt pulse
- SCR latchup, 759
- sequential, **728–745**, 762r
 - miscellaneous, 746
 - timing example, 748
- setup time, 732
 - violation, 733g, 733s, 756n
- shift register, 762r, 1084
 - feedback PRBS, 977
 - linear feedback, *see* LFSR
 - noise source, *see also* LFSR, 558
 - RAM as, 745, 745, 746g
 - timing, 746g
- speed, 710s
 - vs power, 792g
 - vs voltage, 794g
- standard, 763r, 793
 - combinational ICs, 724
 - gates, 715, 716t
 - sequential ICs, 740
 - when to use, 782
- startup reset, 755, 755
- state machine, 734, **734**
 - Mealy, Moore, 736
- states, 704, 797g
- strobe, 725
- SUHL, 790
- switch, **725**, 919t
- switch input as pulldown, 729n
- synchronizer, 737, 738
- synchronous, **734**, 743s, 777
- syntax, 711t
- three-state, 720, 720, 996
- through cables, **850ff**, 879r, **1121**
 - comparison, 867
- timing skew, 737n
- toggling, 196
- toggling flip-flop, 731
 - Verilog code for, 732
- transmission gate, 172, 725, **725**, 919t, 1019
 - bidirectional, 727
- truth table, 708
- TTL, 714, 790–793
 - characteristics, **718ff**
 - noise in, 758
 - output characteristics, 827
 - unspecified rules, 757
 - unused input, 718, 738, 754, 759, 760, 806
 - LVDS trick, 800
 - wired-AND, 722, 1085
 - wired-OR, 721, 722
- lookup table, 735
- loop gain, 117
- loss
 - switching, 662
- loudspeaker
 - as microphone, 486
- low dropout, *see* voltage regulator, low-dropout
- low-voltage differential signaling, *see* LVDS
- LVDS, 705n, 794, 859, **862–864**, 880r, 1033
 - levels, 867
 - power, 868g
 - rates, 867g
 - signal conditioning, 864, 865s
 - torture test, 863, 863s
- LVPECL, 794, 868
- macrocell, *see* programmable logic device (PLD)
- magazines, 1157
- magnet controller, 365
- man
 - transistor, 75
- Manchester code, 1044
- Manchester coding, **1042ff**
- MARK and SPACE, 771n
- Mark (RS-232), 865
- math review, **1101–1104**
- MDAC, *see* DAC, multiplying
- memory, *see also* computer, *see also* logic, *see also* microcontroller, 745, 993, 994, **1017–1030**, 1054r
 - 1T1C cell, 1022
 - 6T cell, 1019
 - burst mode, 1024
 - cache, 993, 994
 - computer, 994
 - configuration, for FPGA, 769
 - double data rate, *see* DDRn
 - dynamic, 994, 1022, **1021–1024**, 1054r
 - asynchronous, 1021, 1023, 1024
 - latency, 1024
 - synchronous, 1024, 1025
 - timing, 1024, 1025

- endurance, 769
- EPROM, 769
- flash, 769, 994, 1085, 1098, 1100r
- HDD, 994
- multilevel cell (MLC), 1028
- non-volatile, 764, 769, 770, 772, 779, 787r, 1054r
- nonvolatile, **1024–1030**, 1070
 - EEPROM, 1026, 1054r, 1056, 1067, 1085, 1087, 1098, 1100r
 - EPROM, 1026
 - ferroelectric, 1025, 1028
 - flash, 1025, **1027ff**, 1054r, 1056, 1093, 1098
 - floating gate, 1025, *1026*
 - JTAG programming, 1039
 - magnetoresistive, 1025, 1029
 - mask ROM, 1026
 - NAND flash, 1027, *1028*
 - NOR flash, 1027, *1027*
 - phase change, 1025, 1029
 - PROM, 1026
- page mode, 1022n
- pseudo-static, 1020, *1020*
- RAM
 - as shift register, 745, 745, 746g
- read cycle, *1020*, *1022*, *1024*, *1025*, 1052r
- retention, 769
- ROM
 - in state machine, 735, 736n
- SSD, 995
- static, 769, 994, *1019*, **1019–1021**, 1054r, 1064, 1098, 1099, 1100r
 - asynchronous, 1019, *1019*, *1020*
 - synchronous, 1021, *1022*
 - timing, 1019, *1020*, *1022*
- static vs dynamic, 1018
- volatile, 994
- volatile/nonvolatile, 1017
- wrapup, **1029**
- write cycle, *1020*, *1022*, *1024*, *1025*, 1052r
- MEMS, 446n
- metastability, *see* logic
- meter, 61
- mho, 6
- microcomputer
 - terminology, 992, 1052r
- microcontroller, 747, 749, 763r, 797, 889, **1056–1098**, 1099r
 - 8051, 1063, *1070*, 1091, 1094p, 1095–1097
 - ac power control (design example), *1066*, **1065–1068**
 - pseudocode, 1067, *1068*
 - ADC timing example, 1092, 1092g
 - pseudocode, 1093
 - ARM, 1039, 1063, 1091, 1094, 1094p, 1095–1097, 1098n, 1099r
 - as debouncer, 803, *804*
 - as timer, 469
 - assembly code
 - for PRBS generator, 783
 - PRBS generator, 779
 - assembly language, 779
 - AVR, 1039, 1058, 1062, 1063, 1091, 1093–1097, 1099r
 - Blackfin, 1064
 - block diagram, *1057*
 - bypassing, 1059
 - C-language code
 - for PRBS generator, 784
 - PRBS generator, 782
 - code download, 1062
 - Coldfire, 1064, 1094p, 1097
 - constraints, 1090
 - debugger, 779, 1099r
 - development environment, **1090–1096**, 1099r
 - cost, 1096
 - development kit, 1094, 1094p
 - firmware, 1059
 - frequency synthesizer (design example), 1070p, **1068–1072**
 - block diagram, *1069*
 - pseudocode, 1070, *1071*
 - how to select, 1098
 - IDE, 779
 - implementing delta-sigma ADC, 934, 935
 - in-circuit debugging, 1096, 1100r
 - in-circuit programming, 1056
 - instrumentation amplifier frontend, *1074*
 - JTAG programming, 1039, 1056
 - loading code on, **1093–1096**
 - JTAG bootloader, 1095
 - parallel bootloader, 1095
 - proprietary bootloader, 1095
 - SPI bootloader, 1095
 - UART bootloader, 1094
 - USB bootloader, 1095
 - logic inputs, 1084, 1087
 - MIPS, 1064
 - MSP430, 1064
 - object code, 779, 1100r
 - output characteristics, 798g

- output current, 798g
- peripheral ICs, **1081–1090**
 - direct connection, 1083, **1082–1085**
 - I²C connection, 1089, **1087–1090**
 - SPI connection, 1086, **1085–1087**
- peripherals
 - on-chip, 1064ff
- PIC, 1063
- popular families, **1062–1064**
- PowerPC, 1064
- PRBS generator, 777ff, 782
- precision ADC in, 1074
- Propeller, 1064
- PSoC, 1064
- Rabbit, 1063
- realtime constraints, 1092
- SH-4, 1064
- simulator, 779, 1099, 1100r
- software, **1090ff**
 - assembly code, 1091
 - assembly language, 1099r
 - BASIC, 1091
 - C/C++, 1091
 - Java, 1092
 - Python, 1092
- special-function register, 779
- ST6/7, 1064
- stabilized platform (design example), **1080**, 1080p, 1082p
 - block diagram, 1081
 - pseudocode, 1081
- suntan monitor (design example), **1057–1062**
 - C-language code, 1061
 - circuit, 1057, 1058
 - pseudocode, 1059, 1060
- terminology, 992
- thermal controller (design example), 1074, **1072–1080**
 - block diagram, 1072
 - control loop, 1077, 1078
 - pseudocode, 1078, 1078
 - when to use, 785, 1097, 1100r
 - wrapup, **1096–1098**
- XMOS, 1064
- microconverter, 1073
- microphone
 - capacitor as, 682
 - loudspeaker as, 486
 - ribbon preamp, 505
- micropower
 - digital design, 753
- microstrip, *see also* stripline, 852, 1121, 1123
- Miller effect, 105, **113ff**, 130r, 197, 197g, 198s, 511
 - and differential amplifier, 114
 - configurations that avoid, 115, 148, 152n
- Millman's theorem, 6, 1112
- mini-logic, 715n, 715p, 772n, 800n
- MiniGate, *see* mini-logic
- mixer, 395, 562, 563, 1143
- M²L, *see* logic, Mickey-Mouse
- modem, 866
- modified sinewave, 673s
- modulation
 - 8-VSB, 1142n
 - 8PSK, 1143
 - amplitude (AM), 55, 56s, 972, 1138
 - homodyne, 972
 - synchronous, 972
 - BPSK, 972
 - delta, 912
 - frequency (FM), 971, 1138
 - demodulation with PLL, 971
 - Foster-Seeley detector, 972
 - quadrature demodulation, 971
 - ratio detector, 972
 - slope detector, 972
 - pulse-code (PCM), 703, 973
 - QAM, 972
 - QPSK, 972, 1143
 - quadrature amplitude (QAM), 1142n
 - synchronous detection, 575, 576
 - video, 1137
- modulator
 - delta-sigma, 926, 927
 - magic in, 929
- monostable multivibrator, *see* one-shot
- monotonicity
 - converter, 882
- Monticelli output circuit, 318, 330
- Moore's law, xxix, 748, 992n, 993p, 1021n
- MOSFET, *see also* FET, 134
 - as pullup, 828
 - avalanche rated, 819n, 1076, 1076
 - construction, 134
 - depletion-mode, 209, 210t, 222r, 698
 - as current source, 622
 - as input protection, 210, 951
 - current source, 211
 - extending regulator V_{IN} , 211, 693
 - HV discharge, 211

- dynamic gate current, 164
- floating-gate reference, *see* voltage reference
- gate capacitance, 197g, **197ff**
- gate driver, 194, *194*, 218t, 753, 797, 798g, 823, 828, 832, 855, 1076, 1099r
 - optocoupler, 206
- gate threshold, 137
- handling precautions, 200
 - gate damage, 201p
- high-voltage
 - creepage barrier, 665p
- lateral, 213
- logic switch, 184
- maximum ratings, 221r
- noise, 519, 520g
- polarity, 134
- power, **187ff**, 188–191t
 - applications, **202ff**
 - body diode, 199
 - drain capacitance, 198
 - floating switches, 205
 - gate breakdown, 199
 - gate capacitance, 197g
 - gate charge, 197g, 198s
 - gate protection, 199
 - high-side switching, **202ff**, *204*
 - high-voltage, 202, 662, 695
 - lateral, 214g
 - light-at-night, 206
 - linear applications, 208
 - logic-level, 192, *193*
 - paralleling, 201, **212ff**, *214*, 222r
 - piezo amplifier, 208
 - piezo driver, 207
 - power rating, 199
 - protected switch, 204
 - push-pull follower, 214
 - source ballasting, 213
 - switch, 206t, 221r, 1076
 - switch examples, 206
 - switching applications, *195*, *196*, 192–196
 - switching cautions, 196
 - thermal runaway in, 214
 - thermal stability, 187
 - vs BJT and IGBT, 201, 202t, 208t
 - R_{ON} vs temperature, 213g
 - R_{ON} vs voltage, 202, 662
- schematic symbols, *134*
- series connection of, 697
- source ballasting, *214*
 - switch, 1084
 - floating, **203**
 - high-side, 825, 826t, 1085
 - protected, 824, 825, 825t, 1085
 - protecting, **823ff**
 - switching examples, *193*, *204*, *205*, *820*
 - transfer characteristics, 212g
 - vs JFET, 170
- motor driver, *1081*, 1082p
- motorboating, 287
- mouse, 1067
- MOV, *see* varistor
- MP3, 1141n
- MPEG, 1097
- MPEG-2, 1141n
- MPEG-4, 1064, 1141n
- MSP430, *see* microcontroller
- multichannel scaling, *see* bandwidth, narrowing
- multimeter, 2, 10 (box)
 - true rms, 631
- multiplex
 - video, 1142
- multiplexer, *see also* logic, 724
 - FET analog switch, 173
 - in DAQ, 948
- multiply
 - how to, *761*
- multiplying DAC, *see* DAC, multiplying
- multislope
 - conversion, *see* ADC
- Nakamura, Shuji, 62
- NAND, *see* logic, *see* memory, nonvolatile
- narrowcast, 1146
- negative-impedance converter, 397
- negative-true, *see* logic
- netlist, *see* programmable logic device (PLD)
- network
 - local-area (LAN), 1049
- NEXT (near-end crosstalk), 581
- night light, 206
- NMR, 577
- node, 2
- noise, *see also* amplifier, *see also* op-amp, 15, 326, **473–481**, 636s, 637
 - 1/f, 590r
 - corner frequency, 566
 - filtered bandwidth, 564t
 - forever?, 566, 567s
 - integrated, 566g

- JFET, 510, 517g
- $1/f$, 337, 476g, **476**, 491, 520
 - cancellation of, 485n
 - op-amp, 324, 324g, 530
- analog
 - filtered PRBS, 977, **979–984**
- averaging time, 574
- band-limited, 477
- bandpass filters
 - response, 565g
- bandwidth, 477, **561ff**
 - multisection RC , 561
 - of LC , 561
 - of an average, 562
- bistable, 477s
- BJT, *see* BJT, noise
 - test circuit, 557
- burst, 477, 477s, 590r
- capacitively coupled, 581
- common-mode choke, 585
- crest factor, 568, 983
- current, **483**
 - measuring, **569ff**
 - of bias-canceled op-amp, **327**, 527
 - ultra-low measurement, 571, 572
- current source, of, **487ff**
- density, 474, **479**, 590r
 - voltage, 481ff
- differential amplifier, 520
- digital
 - generation with PRBS, **976–984**
- emitter follower, **487ff**
- e_n - C , 541, 542g, 542s, 543g
- e_nC , 540g
- e_nC , 532, 538, **538ff**
- equivalent power (NEP), 537n
- exceedance probability curve, 574g
- excess, 475ff, 590r
- figure, **479**, 480g, 493g, 519, 592r
 - contour plot, 490g, 492, 493g
 - conversion to SNR, 480
 - example, 492
- filtered
 - over decades, 567s
- filtering out-of-band, 913
- flicker, *see* noise, $1/f$
- floor, 418
- Gaussian, 475g, 590r, 981, 983
- generator, 559
 - pink, 559
 - pink, spectrum, 560s
 - PRBS, 558
- immunity, 705, 754
- in inverting amplifier, 521
- in noninverting amplifier, 520
- instrumentation amplifier, 362
- integrals, 564t
- integrated
 - calculating, 563
 - of op-amps, 338g, 530, 531g, 531t
- interference as, 478
- JFET, *see* JFET, noise
- Johnson, *see* Johnson noise
- low-frequency specification, 564
- magnetically coupled, 581
- maxima, 574
- measurement, **555ff**, 568, 592r
 - hot-cold, 557
 - RF, 558
 - transistor test circuit, 557
- MOSFET, *see* MOSFET, noise
- mosquito, 1141n
- Nyquist, *see* Johnson noise
- of switching power supplies, 649
- of voltage regulator, 618
 - filterin, 620
 - filtering, 619
- op-amp, 522t, 523t, 524t, 528g, 529g, 532s, **520–533**
 - autozero, **333ff**, 334s, 568g, 570g, 572s
 - choosing, **525–533**
 - spectrum, 568g, 568s, 570g, 572s
 - vs C_{in} , 532g
- peak vs rms, 532, 564, 568, 937n
- phase, *see* phase, noise
- pink, 477s, 559, 563ff, 566
- popcorn, 477s, 478g, 590r
- potpourri, 574
- power supply, **578ff**, 580g, 580t, 593r, 618, 915
 - capacitance multiplier, 557, 578, 579g
- pseudorandom, *see* PRBS
- quantization, 929g
- quantization error, 574
- quick guide to, 473
- red, 477s, 563ff
- rejection in PLL, 976
- resistance, **494**, 501, 502t, 522t, 528, 569, 592r
- rms vs magnitude, 574
- shaping, *see also* delta-sigma, 929, **929ff**
- shot, 327, **475ff**, 476t, 482g, 511g, 590, 591r

- equivalent to Johnson noise, 482, 509, 525n
- suppression of, 476, **487ff**, 488
- source
 - PRBS circuit, 982
- sources, **558ff**, 590r, 592r
- switchmode power supply, 636g, 636s, 637
- telegraph, 477s
- temperature, **480**, 519, 592r
- threshold-crossing rate, 574
- true random, 984, 991r
 - circuit, 986
- types of, 474, 477s, 558, 590r
- units of, 474
- unspecified, 503, 504g, 507, 517, 517g, 519, 535
- voltage
 - from filtered PRBS, **980**
- voltage reference, *see also* voltage reference, 682g, **682**
- white, 474ff, 477s, 563ff
- zener, 676n
- nonlinearity
 - converter error, 882, 901
- nonmonotonicity
 - converter error, 882
- NOR, *see* logic, *see* memory, nonvolatile
- Norton equivalent circuit, 66, 69r, 1112
- NRZ, 1044
- NRZI, 1044
- NTSC, 1065, 1136n, 1138, 1140
- number
 - 2's complement, 707, 1049
 - arithmetic in, 708
 - BCD, 706
 - codes, **705–708**, 882, 1049–1051
 - floating-point, 708n, **1050**
 - formats, 1050
 - formats, 1050
 - Gray-code, **708**, 709
 - binary conversion, 711
 - hex, 705
 - notation, 705
 - integer
 - justification, 1049
 - signed, 707t
 - offset binary, 707
 - sign-magnitude, 707
 - signed, 707
 - storage in memory, 1051
- nybble, 993
- Nyquist, 395, 419
- noise, 474
- Odroid, 1056n
- offline, *see* ac powered
- offset binary, *see* number, codes
- Ohm's law, **4**
 - generalized, 46
 - not obeyed by diode, 31
- one second per hour (design example), 467
- one-shot, 77, 242, 459, 460, 463t, **461–465**, 471r, 739, 762r
 - 555, 460, 460
 - application examples, 465
 - cautions, **462ff**
 - circuit, 461
 - problems with, **462ff**
 - protecting pulsed power devices with, 465
 - reset, 462
 - retriggerability, 462
 - timing coefficient, 464g
- op-amp, **223ff**, 224p
 - 1/f noise, *see* noise
 - absolute-value circuit, 257
 - ac amplifier, 226
 - biasing, 261, 262
 - accuracy vs linearity, 313
 - active clamp, 257, 289r
 - active peak detector, 254
 - active rectifier, 238, 257, 289r
 - effect of slew rate, 238
 - as voltage regulator, 235
 - autozero, 254, 272, 295, **333ff**, 334, 335t, 370, 388, 389r, 935
 - common-mode input range, 340
 - external, 341, 341
 - input current, 339
 - instrumentation amplifier, 342
 - integrated noise, 338g
 - noise, 336g, 336, 337s, 569t
 - noise current, 339, 570g, 572s
 - noise voltage, 339, 568g
 - offset voltage, 339
 - overload recovery, 337
 - selecting, **338ff**
 - self-calibrating, 341
 - settling time, 340
 - slew rate, 340
 - supply voltage, 338
 - bandwidth, 247, 249, 290r, 308, 328, 329g
 - basic circuits, 225–231, 288r

- bias canceled, 125, 252, 266
 - better than JFET, 303g
 - current noise of, 327, 527
- Bode plot, 290r
- capacitive load, 332
 - driving, 264
 - stability, 265g
 - stabilizing, 263s, 264
- cautions, 231, 289r
- chopper-stabilized, *see also* op-amp, autozero, 340, 340, 1073
- clamping, 914
- CMRR, 305, 328
- CMRR and PSRR, 249
- common-mode input range, 245, 290r
 - of autozero, 340
 - of difference amplifier, 354
- compensation, 280ff, 283, 290r, 308
- compensation pin, 320, 321t
 - clamping, 914, 915
- current feedback, 270, 384, 385
 - peaking vs gain-setting R , 379g
- current source, 228–230, 242, 254, 344, 367, 622, 623, 897
 - Howland, 229, 230
- current-to-voltage converter, 233
- decompensated, 283, 283g, 328, 515, 542, 550, 553
- departure from ideal, 243–249, 289r
- detailed look, 242–253
- die (LT1028), 527p
- difference amplifier, 227, 288r, 347–387
 - bandwidth, 355
 - CMRR trim, 356, 357
 - configurations, 356
 - filter node, 355
 - offset trim, 355, 357
- differential amplifier, 347–387
- differential input range, 232, 246, 535
- differentiator, 260, 288r
- distortion, 329ff, 331, 332g
 - slew-rate, 248s
 - vs frequency, 311g
- driving logic from, 808
- feedback at dc, 232
- follower, 227, 288r
 - with bootstrap, 233
- frequency compensation, *see* op-amp, compensation, 247
- gain, 249, 290r
 - vs frequency, 281–284g, 311g, 329g
- gain error, 312, 312g
- gain nonlinearity, 312ff, 313
 - measuring, 313
- golden rules, 225, 288r
- high-power, 272t
- high-speed, 310t
- high-voltage, 272t
- hybrid amplifier with JFET, 151, 153g, 155g, 343, 344, 534, 545
- ideal, 243, 288r
- input
 - protection, 294, 362
- input capacitance, 532
- input current, 163, 244, 252, 289r, 302, 325, 388r, 535
 - BJT better than JFET, 303g
 - common-mode voltage, variation with, 304, 306g
 - effect on integrator, 257
 - measuring, 325ff
 - of autozero, 339
 - temperature, variation with, 303g, 307, 325g, 530
- input impedance, 245, 250, 301, 306
- input offset current, 244, 252
- input protection, 258, 362
- instrumentation, *see* instrumentation amplifier
- integrator, 230, 231s, 257–260, 288r, 935
 - resistor stabilization, 259
- inverting amplifier, 225, 288r, 316n
 - noise, 521
- JFET
 - fast, 155t
- JFET hybrid, *see* op-amp, hybrid amplifier with JFET
- limitations, effect on circuits, 249–254
- linearity, 251
- low input-current, 303t
- low noise, 522–524t
 - choosing, 525–533
 - hybrid, 534
- micropower, 273
- Monticelli output circuit, 318, 330
- noise, 289r, 528g, 529g, 520–533, 592r
 - 0.001–10Hz, $1/f$, $V_{n(pp)}$, 531g
 - 0.01–10Hz, $1/f$, $V_{n(pp)}$, 564
 - $1/f$, 528, 529g
 - autozero, 333ff, 334s
 - impedance, 326
 - integrated, 338g, 530, 531g, 531t

- low-frequency, 530ff, 532s, 564
- measuring, 568
- vs C_{in} , 532g
- noise current, **326ff**, 336g, 530, 570g, 572s
 - measuring, **569ff**
 - of autozero, 339
- noise resistance, 528
- noise spectrum, 568g, 568s, 570g, 572s
- noise voltage, *see also* noise, 323, 324g, 336g, 337, 535, 568g
 - measuring, **567**
 - of autozero, 339
- noise voltage and current, 249, 526
 - of bias-canceled, **327**
 - vs supply current, 525g
- noninverting amplifier, 226, 288r
 - noise, 520
- nonlinear circuits, 236, 289r
- offset trim, 306, 534
- offset voltage, 244, 251, 289r, 304, 306, 323, 388r
 - effect on integrator, 257
 - of autozero, 339
 - test circuit, 323
- offset voltage drift, 244, 289r
- optional inverter, 232
- oscillator
 - precision VCO, 267
- output current, 251, 272t, 290r
- output errors, 389r
- output impedance, 246, 250, 290r, 309
 - effect on MFB filter, 414g
 - effect on VCVS filter, 414g
 - vs frequency, 250g, 311, 312g
- output range, 231
- output swing, **246**, 290r
 - vs frequency, 251g, 307g
 - vs load resistance, 246g
- output voltage
 - vs load current, 247g
- parameters, 245t
 - unspecified, 295
- peak detector, 289r
 - resetting, 255
- phase error, 314, 315g, 315t
 - active compensation, 314, 315g, 315t
- phase reversal in, 275, 361n
- phase shift, 247, 290r
 - vs frequency, 311g
- photodiode amplifier, 233
- photometer, 265
- pinch-off voltage tester, 240
- pinout, 225
- power, 588
- power and high-voltage, 272t
- power booster, 234
- precision, **292ff**, 320, 321t, 388r
 - choosing, 319
 - representative, 302t
 - vs speed, 329
- programmable pulse-width generator, 241
- PSRR, 306, 328, 533
- push-pull booster, 234
- rail-to-rail, 236, 246, 266, 277, 289r, **315ff**, 389r
 - V_{OS} shift, 316g
 - distortion, 317g, 318
 - gain, 318g
 - input circuit, 316
 - input crossover, 316, 317g
 - output circuit, 317
 - output impedance, 316, 318g
 - output saturation, 317
 - output swing, 247g
- relaxation oscillator, *see also* oscillator, relaxation, 425
- representative, 271t
- sample-and-hold, 256, 289r
- schematic
 - LF411, 243
 - TLC271, 266
- self heating, 306
- sensitive millivoltmeter (design example), 253, 293, 296t
- settling time, 308ff, 311g, 320, 321t, 328
 - of autozero, 340
- sign of feedback, 232
- single-supply, 245, 261, 265–270, 289r, 322
- slew rate, 248g, 251, 290r, 307, 328, 329
 - distortion, 248s
 - of autozero, 340
 - vs f_T , 308
 - vs input differential, 308g
- smorgasbord, 232
- split feedback, 263
- stuck-node tracer, 276g
- summing amplifier, 234
- supply rail splitter, 262
 - stability, 263, 263s
- supply voltage, 248, 322
 - of autozero, 338
- supply-rail bypass, 232

- tables of, 271–272t, 296t, 302, 303t, 310t, 320, 321t, 335t, 522–524t
- track-and-hold, 256
- transconductance, *see* OTA (operational transconductance amplifier)
- transimpedance amplifier, *see* transimpedance amplifier
- triangle oscillator, 239
- uncompensated, *see also* op-amp, decompensated, 283
- voltage feedback, 385
- voltage gain, 247
 - vs frequency, 247g
- zero-crossing detector, 269
- open-collector, 721, 799, 807, 811, 817
- open-drain, 721, 799, 807, 811
- optocoupler, 805, 842, 843, 844, 846, **840–846**, 847, 871, 872p, 873, 874, 879r, 917, 1065, 1067
 - analog, 586, **843**
 - as variable resistor, 437, 438n
 - for isolated feedback, 663
 - gate drive, 206, **842**
 - linearizing, 844
 - logic output, **841**
 - photoconductive
 - linearity, 437
 - phototransistor output, **841**
 - signal isolator, 586
- optoelectronics, **829–850**, 878r
 - 16-segment display, 836
 - 5x7 matrix display, 837
 - 7-segment display, 836, 836
 - angle encoder, 879r
 - coupler, *see* optocoupler
 - detectors, **838**, 871p, 878r
 - display
 - LED, multiplexed, 751, 751ff, 836
 - multiplexed, 443, 751, 751
 - display technology, 1146
 - displays, 62, 830p, **835ff**, 871p, 878r, 1084
 - emitters, 830p, **829–838**
 - family tree, 829, 869 (box)
 - fiber optics, *see* fiber optics
 - image sensor, 871p, 1064
 - interrupter, **846**, 872p, 879r
 - IrDA, 1064, 1084
 - laser diode, *see* laser diode
 - LCD, 835, 838, 871p, 1064, 1069, 1099, 1100r, 1146
 - interface timing, 1031
 - LED, *see* LED, 1065
 - LED backlight, 1087
 - LED stick, 837
 - light-to-frequency, 1084
 - miscellaneous, 871p
 - multicharacter display, 837
 - OLED, 835, 1085, 1147
 - optocoupler, *see* optocoupler, 1084
 - photo-Darlington, 839
 - photoconductive, 437, 438n, 872p
 - photoconductive mode, 839
 - photodiode, **839**
 - photomultiplier, 840, **840**, 871p
 - amplifier, 872
 - phototransistor, **839**
 - photovoltaic mode, 839
 - photovoltaic stack, 204, 845, 874
 - PIN diode, 871p, 975
 - plasma, 1147
 - proximity detector, 846, 879r
 - rotary encoder, 1069
 - smart display, 837
 - codes, 838
 - synchronous detection, 578
 - VFD, 835, 1069, 1070
- optointerrupter, *see* optoelectronics
- optoisolator, *see* optocoupler
- orthogonal
 - adjustments, 515
- oscillation
 - damped, 53g
 - parasitic, 426, 427s, 442
 - parasitic oscillations in, 427s
 - slow logic transition, from, 801s
- oscillator, 289r, **425–457**, 470r, 700r, 1084
 - 555, 429, 430t, **428–432**
 - 50% duty-cycle, 429
 - full-range duty-cycle, 430
 - sawtooth, 430, 430
 - triangle, 431, 432
- atomic standard, 451
- blocking, 656
- ceramic resonator, 450, 471r
- Clapp, 440, 441
- CMOS, 426
- Colpitts, 440, 440
- crystal, 439, 443p, **443–450**, 471r, 1066
 - “pulling”, 435
 - a caution, 449
 - circuits, 447, 447

- equivalent circuit, 444
- micropower, 448, 449g
- modules, 449
- series and parallel modes, 444, 444g
- DDS, 451, 453, 455, 471r, 971, 1068, 1085, 1093
- emitter-coupled, 440
- GPS-disciplined, 451, 471r
- Gunn-diode, 434, 435
- Hartley, 440, 440, 442
- inverter chain, 435, 975
- JFET, 155
 - low-noise, 441
 - spectrum, 442g
- jitter, 457, 973
- LC, 439, 470r
 - electrically tunable, 440
- local (LO), 395, 562, 973, 1143
- low-distortion, 437
- MEMS, 962, 973
- not needed in μ C example, 1059
- OCXO, 970
- op-amp
 - triangle wave, 239
- parasitic oscillations in, 426
- Peltz, 440, 440
- phase noise, *see* phase, noise
- phase-shift, 438, 439
- PLL, 452, 471r
- precision VCO, 267
- programmable, 267
- quadrature, 454, 454s, **453–456**, 470r
- quartz crystal, **443–450**
- ratiometric, 431
- relaxation, 267, 432, **425–435**, 470r
 - 555, 429
 - CMOS logic, 426, 427, 559
 - diac, 428
 - high-voltage, 428
 - neon, 428
 - op-amp, 425, 426
 - unijunction, 427, 428
- resistor-programmed, 433, 433g
- ring, 962
- SAW, 450, 471r, 962, 973
- sawtooth, 430, 430, 919, 920
- silicon, 432, 433t
- sinewave, **435–443**, 470r
 - Wien bridge, **436ff**, 437, 470r
- TCXO, OCXO, 450, 471r
- triangle, 239, 267, 431, 432
- tuning-fork, 441
- types, 452t
- varactor-tuned, 441
- VCXO, 446, 471r, 962, 967, 971, 973
- voltage-controlled, 267, **434ff**, 470r, 961
 - in PLL, **961**
 - with integrated divider, 434
 - YIG, 434, 435
- oscilloscope, 2, **1162ff**
 - analog, 1163
 - digital, 1156, **1166ff**, 1167
 - aliasing, 1168
 - dead time, 1168
 - hints, 1164
 - probe, 67, 1164, 1165
 - active, 809, 809s, 810p, 1165
 - current, 1165
 - skew, 1168
- OTA (operational transconductance amplifier), 100
- output
 - comparator stage, 811
 - comparator swing, 810
 - creating differential, 372
 - current, comparator, 811, 811g
 - current, op-amp, 272t
- output current
 - critical, in SMPS, *see* switchmode
- oven, 450, 681
- overcompensation, 286
- oversampling, *see* sampling
- overtemperature
 - sensor, *see also* sensor, 13, 14, 203, 602, 604, 604 (box), 608, 671
 - absent, 695
- overvoltage, 691
- packet, 1142
 - switching, 1145
- PAL, *see* programmable logic device (PLD), 1065
- PALASM, *see* programmable logic device (PLD)
- parallel, 2
 - bootloader, 1095
 - capacitors, 21
 - conversion, *see* ADC
 - impedances, 46, 69r
 - JFETs to reduce noise, 509
 - MOSFETs, 201
 - port, 1002–1005, 1066, 1069, 1070, 1072, 1084, 1087, 1099r
 - resistors, 5

- resonant crystal mode, 444, 444g, 446g
- parameters
 - unspecified, 295
- parity generator, 728
- PC104, *see* computer, data bus
- PCB
 - ground plane, 759, 852
 - ground wiring, 758
- PCI, *see* computer, data bus
- PCIe, *see* computer, data bus
- PCM, *see* modulation, pulse-code
- peak detector
 - active, 254, 255
 - passive, 254
- PECL, 868
- permeability, 29
- perpetual-motion, 116
- PGA, *see* amplifier, programmable gain
- phase
 - control in DDS, 1071
 - detector, *see also* PLL, 575
 - equalizer, 415
 - error
 - of op-amp, 314, 315g, 315t
 - noise, 968, 970, 973
 - sequence filter, 455, 456, 456g
 - shift, *see* phase shift
 - splitter, 105
 - with discrete BJTs, 88
- phase margin, 247, 263, 276, 282
- phase shift
 - and feedback stability, *see also* Bode plot, **281–285**, 285
 - control in SMPS, 659
 - filter comparison, 404g
 - oscillator, 438
 - RC lowpass, 50g
- phase shifter
 - constant-amplitude, 89, 89
- phase-locked loop, *see* PLL
- phason, 52g
- phasor, 51, 89
- photoconductive mode, 537n, 839n, 869
- photocoupler, *see* optocoupler
- photodiode, **839**
- photometer
 - single-supply, 265
- photomultiplier, 840, **840**
 - amplifier, 872
- photoresistor, 206, 872p
- phototransistor, **839**
- photovoltaic
 - stack, 204, 845, 874
- photovoltaic mode, 537n, 839, 869
- PHY, 865
- pi network, 1113, 1128
- PIC, *see* microcontroller
- pickup, 59, 442
 - common-mode, 583
- PicoGate, *see* mini-logic
- PID loop, *see* feedback
- piezo, 24, 1057, 1058
- piezo driver, 207, 333
- piezoelectric effect
 - capacitor, in, 682n
 - crystal, 443
- PLA, *see also* programmable logic device (PLD)
- platinum RTD, *see* sensor, temperature
- PLD, *see* programmable logic device (PLD)
 - noise generator, 983
 - output characteristics, 798g
- PLL, 435, 452, 974t, **957–976**, 989r, 1069, 1075
 - AM demodulation, 972
 - block diagram, 958
 - Bode plot, 963g, 965g
 - BPSK demodulation, 973
 - capture and lock, **966**
 - capture transient, 966, 967
 - clock generation, 974, 1075
 - “cut and try”, 965
 - design, **962–966**
 - first-order loop, 962
 - FM demodulation, 971
 - frequency multiplier (design example), **963–966**
 - circuit, 964
 - frequency synthesis, 442, **968–971**
 - fractional-*n*, 968, **968**
 - rational-approximation, 970, **970**
 - laser offset locking, 975, 975
 - loop
 - block diagram, 963
 - loop filter, 395, 962, 963, 990r
 - loop gain, 964, 964 (box)
 - loop stability, 962, 963
 - phase detector, 959, 959g, **959ff**, 959t, 960g, 960s, 961g, 989r
 - anti-backlash, 961
 - backlash, 960
 - dead zone, 960
 - pulse synchronization, 973

- rejection of noise and jitter, 976
- sampling clock, 909
- second-order loop, 962
- signal regeneration, 973
- some realities, 966
- spur removal, 395
- VCO, **961**
 - 4046-type, 961, 961s
 - VCO variability, 966
 - with JFET oscillator, 394
- PMT, *see* photomultiplier
- pod, 745, 769, 1039, 1056, 1062, 1094, 1095, 1100
- polar coordinates, 1102
- pole, 52, 69r
- POP, 998
- popcorn
 - noise, 477, 478g
- positive-true, *see* logic
- pot, *see* potentiometer
- pot core, 29, 581
- potential difference, *see* voltage
- potentiometer, 7, 8p, 63
 - digital, *see also* EEPOT, 63, 184, 412, 1085
 - taper, 739
- power, 2
 - ac detect, 1084
 - ac monitor, 1085
 - an hour of (design example), 466
 - density
 - battery vs capacitor, 690g
 - design, **623ff**
 - dynamic, 754
 - entry module, 629, 630, 631, 699r
 - factor, 47
 - correction in offline SMPS, 668, 699r
 - in offline SMPS, 661, 699r
 - in unregulated supply, 635
 - five minutes of, 196
 - in reactive circuits, 47
 - in resistor, 6
 - micro, *see* micropower
 - minimizing, in CMOS design, 754
 - one minute of, 23
 - phantom, 1049n
 - precision source, 285
 - semiconductor packages, 628, 629p
 - spectrum
 - from PRBS, 979, 981g
 - supervisor, 613, 691, 755, 755, 803, 1082
 - switching, 755
 - from logic levels, 192
 - with MOSFETs, 192–200
 - with outboard driver, 237
 - tradeoffs
 - noise, 483g, 509g, 525g
 - speed, 792g
 - train, *see* switchmode (SMPS)
 - transfer, 11
 - transistor, **624ff**
 - series connection, 697
- power supply, *see also* voltage regulator, **594ff**, 595p
 - auxiliary, 668
 - clamp, 692
 - commercial modules, **684**, 685p
 - current limit, 597
 - foldback, 693, 694, 694g
 - of outboard pass transistor, 695
 - favorites, 1156
 - filtering, 32
 - flying capacitor
 - droop, 639g
 - ripple, 639g
 - high voltage, **695ff**, 696
 - kick-start, 669
 - linear
 - compared with switchmode, *see also* switchmode, 635ff
 - topology, compared with SMPS, 630
 - low noise, 915
 - noise, *see* noise, power supply
 - offline, *see* switchmode, offline
 - overvoltage protection, 598, **690ff**
 - power-factor correction, 661
 - rectifier, 634
 - damping spikes, 634
 - regulated, 123
 - regulator, 34
 - resonant charging, 40
 - ripple voltage, 33
 - sequencing, 914
 - spike, 635n
 - spikes, 633n, 634
 - split, 34, 630, 639
 - storage capacitor, 633
 - ripple current in, 634
 - supervisor, *see* power
 - switchmode, **636ff**
 - ac-powered, *see* switchmode, offline
 - compared with linear, 630, 635ff
 - controller ICs, 658t

- current-mode ICs, 654t
 - programmable, 1090
 - voltage-mode ICs, 653t
- uninterruptible, 673
- unregulated, 630, 699r
 - bench vs SPICE, 634, 635s
 - from ac powerline, **628ff**
 - power factor in, 635
- voltage multiplier, 34
- powerline
 - capacitor, 631
 - discharge resistor, 632
 - controller, 1066
 - entry, 629
 - filter, 631
 - monitor, 1085
 - monitor IC, 945, **945**
 - monitor ICf, 945
 - rejection in integrating ADC, 916, 936
 - switch, 631
 - transformer, 632
 - leakage inductance in, 633
 - rating, 632
- PRBS, **558ff**, 762r, **770–782**, **976–984**, 990r
 - 8051 assembly code for, 783
 - ABEL code for, 776
 - analog noise from, 977, **979–984**
 - analog noise voltage, **980**
 - C-language code for, 784
 - chipping sequence, 977
 - digital
 - filter, 981
 - eye diagram, 865s
 - feedback shift register, 977, 978, 981
 - properties, 978
 - taps, 978t
 - noise generator, 559, 771
 - spectrum, 560s
 - noise source
 - circuit, 982
 - power spectrum, 979, 981g
 - Verilog code for, 778
 - VHDL code for, 780
 - with cPLD, 772
 - with discrete logic, 559, 771, 772
 - with ECL logic, 983, 985p
 - with microcontroller, **777ff**, 782
 - assembly code, 779, 783
 - C-language code, 782, 784
 - with PLDs, 983
 - wrapup, 983
- pre-emphasis, 858, 864, 864, 865s, 867g
- precision
 - vs dynamic range, 292, 388r
- prefixes, 4 (box)
- printed circuit
 - SMT vs through-hole, 268, 269
- printer port (Centronics), *see* computer, data bus
- priority encoder, *see* logic
- probe
 - active, 810p
 - for logic signals, 808, 810p
- probing
 - digital signals, 808, 809s, 810p
- program
 - multiplex video, 1142
- programmable (with voltage)
 - current source, 228–230, 367, 898
 - oscillator, 267
 - power supply, 605, 607, 610
 - pulse generator, 920
 - timer (one-shot), 242
 - voltage source, 195
- programmable logic device (PLD), *see also* logic, 728, 737, 745, 763r, 765p, 787r, **764–789**, 797, 1039
 - ABEL, 764, 775, 776
 - address decoder, 1003
 - advice, **782ff**, 788r
 - applications, 787r
 - cPLD, 764, 766, 789r
 - PRBS bit generator, **772–777**
 - CUPL, 764
 - FPGA, *see also* FPGA, 764, **768**, 787r, 1034
 - configuration memory, 769
 - logic element, 770
 - GAL, 764
 - HDL, 745, 764, 765, 787r
 - behavioral coding, 777, 778
 - structural coding, 777, 779
 - HDL entry, **775ff**, 787r
 - advantages, 777, 787r
 - in-circuit programming, 764, 769, 774
 - macrocell, 764
 - mixed-signal, 769
 - netlist, 769, 787r
 - packages, 765p
 - PAL, 764, **765–768**
 - circuit, 766, 767
 - macrocell, 768

- PALASM, 764
- PLA, 768
- place and route, 769, 773, 787r
- pod, 745
- programmer, 769, 773
- programming, 787r
- schematic entry, 745, 773, **773ff**, 774, 787r
 - advantages, 775, 787r
 - software, 769
 - Verilog, 775, 778
 - VHDL, 775, 777, 780
 - WebPACK, 770n
 - when to use, 782ff
- programmable oscillator, 267
- propagation time, 710
- protection, input, *see* input protection
- pseudo-differential, 275, 583
- pseudo-op, 999
- pseudo-random bit sequence, *see* PRBS
- pseudocode, 1059
- PSoC, *see* microcontroller
- PTAT, *see also* bandgap, 92n, 104, 431n, 604 (box), 606, 621, 679, 680
- pullup
 - active, 270, 717, 720, 721
 - current-source, 85, 696
 - passive, 185
 - resistor, 5 (box), 185, 209, 237, 623, 712, 720, 721
- pulse, 16
 - code, *see* modulation, pulse-code
 - duty-cycle
 - limiting, 465
 - forming network, 1130
 - from step, 77, **458ff**, 459s
 - generator, 17
 - high-voltage, 333, 919, 920
 - long pulses, 740
 - n*-pulse, **752**, 753
 - programmable pulse-width, 241
 - single, 739
 - single-pulse, 739
 - triggerable (design example), 739, 740
 - with discrete BJTs, 77–79
 - with flip-flops and counters, 739
 - height analysis, 916
 - limiting width of, 465
 - runt, *see also* logic, *see* runt pulse, 757
 - spectrum of, 943g
 - stretcher, 194
 - synchronization
 - with PLL, 973
 - width modulation, *see* PWM
- PUSH, 998
- push-pull
 - BJT output stage, 81, 106–108, 129r
 - biasing, 108
 - crossover distortion, 107
 - thermal stability of, 108, 214
 - MOSFET output stage
 - thermal stability of, 214
 - op-amp power booster, 234
- PWM, *see also* switchmode, 470r, 645, 699r, 1064, 1065, 1075, 1080, 1098, 1099, 1100r
 - analog vs digital, 1075, 1075
 - as digital-to-analog converter, 890, 890, 892, 987r
 - digital, 1075
 - in class-D amplifier, 109s
 - in switchmode converters, 642, 645ff, 656, 665
 - in thermal control, 1073
 - light dimming, 870
 - rate multiplier as, 892
 - thermal controller, **1072–1080**
 - to DAC converter, 891
 - torque-motor control, 892
- pyroelectric
 - detector, 871p
- Q
 - of crystal, 443
- Q (quality factor), **53ff**
 - spoiling, 53
- QAM, 456
- quadrature, 395n
 - encoder, 847, 872p, 1069
 - FM demodulation, 971
 - oscillator, 454, 454s, **453–456**, 470r
 - RF, 455
 - square waves, 455
- quadrature-amplitude modulation, *see* QAM
- quantization
 - noise, 929g
- R–2R*, *see* ladder
- Rabbit, *see* microcontroller
- radio
 - AM, 55, 56s
 - waveform, 55g
 - waveforms, 56s
- radiofrequency, *see* RF
- rail splitter, 262, 277

- rail-to-rail, *see* op-amp
 ramp, 15
 generator, 27
 random walk, 983
 RAS, 1022
 Raspberry Pi, 1056n
 raster, 1136
 rate multiplier
 as PWM, 892
 ratiometric, 431, 739, 1075
 r_{bb} , *see* BJT (bipolar junction transistor)
 reactance, **40ff**
 graph of, 49g
 reactive circuits, **40ff**
 power in, 47
 read cycle, *see* memory; computer, programmed IO
 reading and references, **1158ff**
 rectification, **31ff**
 rectifier, *see also* diode, 12, **31ff**, 32t, 634
 active, 238
 bridge, 32, 33, 699r
 fast-recovery, 670
 forward drop, 31
 full-wave, 32
 active, 257
 full-wave center-tapped, 33
 half-wave, 32
 power supply
 spikes, 633n, 634
 signal, 35
 soft-recovery, 670
 reference
 design, 671
 reflection coefficient, 1121
 refresh, *see also* memory, dynamic
 display, 1004
 register, *see* logic
 regulation
 cross, 672
 line, 595n
 load, 595n
 secondary, in SMPS, 671
 regulator, *see* voltage regulator
 series pass, 598
 relay
 driver, 194
 driving from logic, 817ff
 electromechanical, 59, 818
 latching, 459, 515, 819
 low-level, 515
 optocoupled, **840ff**
 solid-state, *see* SSR
 reset
 logic startup, 755, 755, 1082
 of core, in SMPS, 657
 resistance
 dynamic, 12
 internal, 10
 leakage, 10
 negative, 7, 397, 646, 650n, 1117
 noise, *see* noise resistance
 of analog switch, 175, 950n
 small-signal, 12
 source, 10
 thermal, *see* thermal resistance
 resistor, **3ff**, 3p, 5 (box), 68r
 4-wire, 294n
 accuracy, 1110t
 bleeder, 634
 chip
 sizes, 4n
 color code, 1109t
 current-sensing, 754, 760
 digital, 1085
 discharge, for powerline capacitor, 632
 E96 series, 1108t
 emitter-ballasting, 113
 excess noise in, 476
 high-voltage, 698
 in parallel, 5
 in series, 5
 international notation, 5n
 Kelvin, 350
 noninductive, 696
 nonlinearity, 697, 1110t
 power in, 6
 power package, 3p
 precision, 293, 300, 345, 348–350, 696
 precision divider, 679
 properties of, 300, 388r
 pullup, 5 (box), 209, 237, 623, 720, 721
 logic input, 805
 MOSFET as, 828
 on demultiplexer, 727
 standard values, 1108
 suppression, 573
 T-network, 259
 tempco, 300, 679, 1110t
 types, **1108ff**, 1110t
 variable, 63

- JFET, 161
 - stability, 679
 - voltage coefficient, 697, 1110t
 - voltage rating, 697
 - wirewound, 3p, 8p, 1073, 1109
- resonant
 - charging, 39, 40
 - circuit, 52ff
- reverse polarity protection, 616, 665, 671
- RF
 - driving cable, 856
 - noise measurement, 558
- RFI (radiofrequency interference), 582, 668
- ribbon microphone, 505
- ringback, 759
- ringing
 - capacitive loads, 263s, 264
 - in SMPS, 668, 668n
 - logic signals, 809s, 850ff, 879r
- ripple, 635s, 639g, 699r
 - current, 644
 - effect of capacitor ESR, 639n
 - effect of switchmode frequency, 641
 - filtering, 619
 - in unregulated supply, 599, 632
 - of filter, 399
 - switchmode power supply, 636s
- rise time, 16
 - of RC, 22
 - of filter, 400
- RLL, 1044
- Rogowski coil, 946, 946
- rotary encoder, 1069
- RS-232, *see also* computer, data bus, 771, 866s, **864–867**, 1041, **1041ff**, 1042s, 1064–1066, 1069, 1084, 1093, 1099r
 - and cable length, 867
 - driver ICs, 865
 - levels, 867
 - mark, 1041
 - power, 868g
 - pseudo-random byte generator, 770
 - rates, 867g
 - signals, 1042t
 - START bit, 1041
 - STOP bit, 1041
 - timing ambiguity in, 1041
 - to USB adapter, 865n, 1067
- RS-422, 859, 859, **859ff**, 860s
 - levels, 867
 - power, 868g
 - torture test, 860, 860s
- RS-485, 859, **859ff**, 860s, **1041ff**, 1064
 - isolated, 861, 876
 - levels, 867
 - power, 868g
 - rates, 867g
- RTC, 1087
- RTD, *see* sensor, temperature
- rubidium, *see* oscillator, atomic
- runt pulse, *see also* logic race, 738, 743s, 748, 753n, 757
- s*-plane, 52
- S/PDIF, 1064
- safe operating area (SOA), 113n, 192g, 216, 603n, 604 (box), 627, 702r
- Sallen and Key filter, 399, 409
- sample
 - PLL clock, 909
- sample-and-hold, *see also* op-amp, 183, 256
- sampling, 419, **902ff**, 903, 909
 - bandpass, 909
 - depth
 - and dynamic range, 902
 - direct IF to digital, 909
 - images, 933g
 - Nyquist criterion, 902, 903
 - over, *see also* delta-sigma, 903, 903, 904n, 926, 930
 - ratio (OSR), 926
- rate
 - and aliasing, 902, 903
 - and bandwidth, 902
 - rate and aliasing, 933g
 - under, 903, 909
 - band conversion, 909
- SAS, *see* computer, data bus
- SATA, *see* computer, data bus
- satellite
 - geostationary, 1143
- saturation, *see* BJT, *see* FET
 - in BJT, 73
 - Schottky clamp prevents, 717n
 - of magnetic core, 657, 659
- sawtooth, *see* oscillator
- scaling
 - of IC feature size, 793n
- scary stuff, 1028
- schematic
 - diagram

- how to draw, **1105ff**
 - entry
 - in SPICE, 1150
 - ugly, *1106*
- Schmitt trigger, 128r, 237, 237g, 267, 269, 270, 279, 279, 289r, 459, 717, 754, 755, 801, 801s, 803s, 805, 807, 807, 808s
 - logic input, 801, 801s, 802
 - speedup capacitor, 808s
 - transfer function, 237g
 - with discrete BJTs, 79
- SCPI, 1068n
- SCR, *691*, 1065
 - latchup, 759, 795
 - overvoltage crowbar, 598, 672, **690ff**
- SCSI, *see* computer, data bus
- SD card, 1085
- SDR, 1024
- second breakdown, 113n, 187, 216, 627, 702r
- Seebeck effect, *see* thermal EMF
- sensor
 - ac power, *945*, *946*
 - acceleration, 1080, 1082p, 1085, 1087, 1099r
 - atom, 553ff
 - charge, *935*
 - current, *945*, *946*
 - force, 1080
 - grasp, *372*
 - gyro, 1080
 - inductance, 1087
 - light, *498*, *548*, *578*, 871, 872p
 - lightning, *497*
 - magnetic field, 1085
 - proximity, 1087
 - rotation, 1080, 1085, 1099r
 - sound, 486, 505ff
 - strain, 297ff, 347, 348, 588, 939
 - suntan, **278–280**, 924, **1057–1062**
 - temperature, 13, *14*, 671, 1073
 - RTC, *1074*
 - RTD, 347, 1073, 1073n
 - semiconductor, 621, 680, 1073
 - thermistor, 123, 372, 661, 1073
 - thermocouple, *see also* AoE 2nd ed., pp 988–992, 337, 341t, 367, 675n, 939, 1073, 1087
- SERDES, 849, 863, 864, 868
- serial, *see* computer, data bus, *see* logic
- series, 5
 - capacitors, 21
 - impedances, 46, 69r
 - resistors, 5
 - resonant crystal mode, 444, 444g
- series-feedback pair, 122, 286
 - with JFET, 150, 151g
- servo, *1072*, 1077
- settling time, 309g
 - of RC lowpass, 309g
 - of filter, 400
 - of op-amp, 308ff, 320, 321t
- setup time, *see* logic
- SH-4, *see* microcontroller
- shielded twisted-pair, *see* STP
- shielding, 579ff, 581, 593r
 - magnetic, 581
- shift register, *see* logic
- shoot-through, *see* current
- shootout
 - ADCs, SAR vs $\Delta\Sigma$, 941
 - at the ADC corral, 941t
 - JFET vs BJT, 517
 - low-power ADC, 943
- shot noise, *see* noise, shot
- shrinkage factor, 391n
- shunt, 294n
 - current, 277
- siemens, 6, 90n, 147
- signal
 - amplitude, 68r
 - averaging, 575, 576
 - bandwidth reduction by, 562, 575
 - differential, 347ff, 705n
 - generator, 17
 - guard, 358, 360, 587
 - mixed
 - PLD, 769
 - protector, *175*
 - regeneration
 - with PLL, 973
 - sampling, 419
 - single-ended, 347, 705n
 - slew rate of, 362
 - to-noise ratio, *see* SNR
 - transformer, *see* transformer
- signals, **13ff**
- Silicon Valley
 - law of, 750g
- silicon-controlled rectifier (SCR), *see* SCR
- SIM Card, 1064
- simulation, *see* SPICE
- SINAD, 987r

- sinewave, 14
 - 3-level, 673
 - arbitrary phase, 456
 - from square wave, 394s, 435, 436s
 - inverter, 673s
 - modified, 673, 673s
 - oscillator, *see* oscillator, sinewave
- Single Gate, *see* mini-logic
- single pulse, 739
- single slope
 - conversion, *see* ADC
- single-ended
 - logic signal, 705n
 - signal, 347
- sizzle test, 625
- skepticism
 - of fourth fundamental element claim, 18n
 - of parts-per-billion claim, 437
- skin depth, 1126g
- slew rate, *see also* op-amp, 328
 - and jitter, 457
 - causes interference, 581, 587, 705
 - filtered, 1076
 - in oscillators, 426
 - of composite amplifier, 922
 - of current source, 367
 - of differential amplifier, 385
 - of op-amp, 248, 307, 328, 329, 515, 857
 - of signal, 362
 - reduced, 607, 650, 759, 820, 860, 865
 - too slow, 757, 808
- slope
 - compensation, 650
- small-signal, 12, **80**, 147
 - impedance, 81, 245
 - symbol for, 80, 90, 1101
 - transistor, 74t
- SMBus, 1064
- Smith chart, 1125
- smoke, 672n
- smoothness
 - silky, 505n
- SMU, 554, 1119
 - favorites, 1156
- SNR, **478ff**
- snubber, 39, 630, 634, 656, 659, 660, 669
- SOA, *see* safe operating area
- SoC, 1034
- soft start, 606n, 607, 645, 650
- solar cell, 2
- soldering iron
 - favorite, 1156
- solenoid, 29
- sound pressure level (SPL), 505ff
- source
 - degeneration, 148, 159, 160, 169, 346, 367
 - sinewave, 41
- source follower
 - JFET, **156ff**
 - gain, 157
 - input impedance, 157
 - low distortion, 160, 161g
 - output impedance, 157
 - tutorial, 159
 - with active load, 158
 - operating point, 156
 - output impedance
 - vs BJT follower, 157
 - push-pull power MOSFET, 214
- source-measure unit, *see* SMU
- source-measure unit (SMU), 899
- Space (RS-232), 865
- SparkFun, 1085
- Sparkfun, 1099r
- spectrum
 - analyzer, 567
 - spreading, 649, 977
- SPI, *see also* computer, data bus, 889, 1031, 1033, **1035ff**, 1064, 1069, 1084, 1090, 1091, 1098
 - ADC SAR example, 911
 - bootloader, 1095
 - bridge, 1087
 - in ADC, 939, 945, 947
 - in DAQ, 948, 949, 956
 - isolation in DAQ, 952
 - microcontroller peripherals, 1086, **1085–1087**
- SPICE
 - amplifier analysis, 1152
 - amplifier analysis, 314, 315g
 - comparison with bench, 459s, 635s
 - crystal analysis, 444ff, 445, 446g
 - filter analysis, 393g, 399g, 414g, 456g, 560g
 - fun with, 93n
 - MOSFET models, 168n
 - power supply analysis, 633–635, 635s
 - primer, **1150ff**
 - pulser analysis, 459s
 - simulation
 - comparison with bench, 1152s
 - transistor model, 482n

- unregulated power supply
 - bench comparison, 634
- spike, *see also* charge injection, 17
 - differentiated edge, 26s
 - from discharge, 200
 - from flyback, 38, 193
 - from hard switching, 668
 - from leakage inductance, 669
 - from snapoff, 199, 633n, 634
 - ground-current, 850
 - in frequency domain, 980
 - in power supply rectifier, 633n, 634
 - in SMPS driver, 669, 669
 - logic driving capacitive load, 851, 851
- spur, *see* frequency
 - removal, 394
- square wave, 16
 - converting to sinewave, 394s
 - quadrature, 455
- SRAM, *see* memory, static; computer
- SSR, 24, 59, 823, **844ff**, 846, 874, 877r, 879r, 1065, 1066, 1084, 1099r
 - leakage current, 1065
- stabilized platform
 - microcontroller, **1080**, 1080p, 1082p
 - microcontroller (design example)
 - block diagram, 1081
- standing-wave ratio, *see* VSWR
- star network, 1045
- START and STOP, 771
- state machine, *see* logic
- state-variable filter, 410ff
- status bit, *see* computer, programmed IO
- status register, *see* computer, programmed IO
- step, 17
 - response
 - filter comparison, 405g, 406t
- stepping motor, 1087
- STM (scanning tunneling microscope), **553ff**
 - image of Si crystal, 554p
- STP, 583, 1121
- stripline, *see also* microstrip, 456, 852, 865s, 1121, 1123n
- stuck node
 - tracer, 276g
- subroutine, 999
- successive approximation, *see* ADC
- suntan monitor
 - delta-sigma, 924ff
 - microcontroller, **1057–1062**
- op-amp, current divider, 279
- op-amp, integrating, 278
- op-amp, two-step, 279
 - with ADC, 924
 - with microcontroller, **1057–1062**
- superbeta, *see* BJT
- supervisory, *see* power, supervisor
- surface acoustic wave, *see* oscillator, SAW
- surface-mount technology (SMT), 3p, 65, 66p, **268**, 269, 432n, 601, 603, 627p, 789r, 793, 1108
 - sizes, 4n, 269n
- surrent
 - sensing, 278
- susceptance, 90n
- sweep generator, 17
- switch
 - 3-way, 59
 - analog, *see* analog switch, 948
 - multiplexer, 948
 - as digital input, 802, **802**, 1084
 - bounce, 729, **802**, 802, 803s
 - break-before-make, 179, 922
 - cold-weld sticking, 573
 - debouncer, 753, 802s
 - built-in, 803
 - clocked, 803, 803
 - keeper circuit, 803
 - latch as, 730, 802, 803
 - slowdown plus Schmitt, 802, 803, 803s
 - software, 803, 804
 - SR flip-flop, 802, 802
 - SR flip-flop as, 730
 - supervisor as, 803
 - debouncing, **729**, **802**
 - DIP, 57p
 - dry-switching, 58, 804, 817
 - floating, 203
 - form A, 58, 803
 - form C, 58, 803
 - high-side, 825, 826t
 - matrix, 1071, 1072, 1084, 1099r
 - mechanical, 56, 57p
 - MOSFET, *see* switchmode; MOSFET
 - opto-interrupter, **846**
 - PCB-mounting, 57p
 - powerline, 631
 - protected, 175, 824, 825t
 - protecting, **823ff**
 - pushbutton, 58
 - reed, 573

- rotary, 58
- self-wiping, 804
- simple logic with, 58
- SPDT, 56, 58, 803
- SPST, 56, 58, 803
- T-switch, 179
- toggle, 57p
- toggling, 195
- switched-capacitor
 - filter, **415ff**
 - integrator, 416
 - resonator, 454
- switching
 - active, 32n, 643
 - amplifier, 109, 109s, 673
 - cold, 75, 725
 - hard, 659, 671
 - high-side, 77, 193, 195, 196, 820, 820ff, 821, 821, 823, 825, 826, 828
 - loss, 662, 671, 1076
 - soft, 671
 - synchronous, 643
- switchmode (SMPS), *see also* voltage regulator, 609, **636ff**, 699r
 - Ćuk, 649, 700r
 - basic topologies, **641ff**, 642
 - boost, 30, 647, **647**, 700r
 - bridge converter, **659**, 700r
 - buck, 30, **642ff**, 700r
 - intrinsically regulated, 643
 - buck, examples, 644ff, 645, 646
 - buck-boost, 649, **651**, 700r
 - burst mode, 643n
 - compared with linear, 630, 635ff
 - continuous-conduction mode, 644, 670n
 - controller ICs, 658t
 - core
 - gapped, 656, 670
 - core reset, 657
 - critical conduction mode, 643
 - critical output current, 643
 - cross regulation, 672
 - current discontinuity in, 649, 651
 - current pulsation, 649–651
 - current-mode, 642, 649, 651, **651ff**, 701r
 - pros and cons, **652**, 701r
 - current-mode ICs, 654t
 - design equations, 644, 647, 648, 656, 657, 659
 - discontinuous-conduction mode, 645, 666, 670
 - duty cycle, 643
 - efficiency, 636, 637, 646, 672
 - feedback stability, 650, 669
 - flux balance, 659
 - flyback, **655**, 657, 665, 700r
 - power train, 671
 - transformer in, 670
 - forward converter, **656**, 700r
 - H-bridge, 655, 659
 - hysteretic, 644, 644, 700r
 - inductorless, **638ff**, 639g, 640t, 699r
 - regulated, 641
 - ripple, 639n, 641
 - internally compensated, 645ff
 - inverting, 648, **648**, 700r
 - isolated, **653ff**, 700r
 - flyback, 655
 - topologies, 655
 - LED driving, 831
 - loss, 662
 - low-noise, 649, 673n
 - minimum output current, 643, 672
 - negative input resistance, 646, 650n, 672
 - noise, 636s, 637, 649, 672, 673n
 - noise spectrum, 636g
 - non-isolated, **641ff**, 642
 - boost, 647, **647**
 - buck, **642ff**
 - buck, examples, 644ff
 - buck-boost, 651
 - design equations, 644, 647, 648
 - hysteretic, 644
 - internally compensated, 645ff
 - inverting, 648, **648**
 - waveforms, 643, 647, 648, 652
 - wrapup, **649ff**
 - offline, 637, 656, 657, **660ff**
 - dual-voltage, 660
 - feedback, 662
 - input filter, 646, 650n, 660, 661, 665, 668, 672
 - input transient, clamp, 669
 - inrush current, 661, 668
 - power-factor correction (PFC), 661, 661, 662s, 668
 - real-world example, **665ff**
 - safety, 672
 - when to use, 672
 - wrapup, **672**
 - phase-shift control, 659
 - point-of-load, 637n, 685
 - PWM, 659, 701r

- PWM modes, **651ff**
- regulation, *630, 637, 637, 641, 642, 645, 646, 649–651, 656, 657, 659, 659, 662, 665, 671, 672, 700r*
- ringing, *667s, 668*
- ripple, *636s, 642, 645, 646, 649*
- SEPIC, *649, 700r*
- slope compensation, *650*
- soft start, *650*
- synchronous switching in, *643*
- topologies, *638, 700r*
 - compared with linear, *630*
- transformer in, *653*
- voltage-mode, *642, 649, 651, 651ff, 701r*
 - pros and cons, **652**
- voltage-mode ICs, *653t*
- waveforms, *643, 647, 648, 652, 666, 667s*
- wrapup, non-isolated, **649ff**
- zero-current switching (ZCS), *650, 659*
- zero-voltage switching (ZVS), *650, 659, 671*
- synchronous, *see also logic, see also memory, 1021*
 - switching, *see switching, synchronous, 32n*
- synchronous detection, *see bandwidth, narrowing*
- synthesizer, *see also frequency, synthesizer, 17*
 - clock, *1087*
- Sziklai, *see BJT*
- T network, *259, 1113, 1128*
- tables, *see Table of Contents*
- take-back-half, *1078*
 - convergence, *1079g*
- tape
 - electrical, *63p*
 - helical, *1139*
 - Kapton, *626*
- taper, *739*
- TCP/IP, *1098, 1144*
- Teensy, *1056n*
- Teflon, *299n, 301g, 326*
- television
 - analog
 - broadcast, *1138*
 - recording, *1139*
 - spectrum, *1140s*
 - cable, *1138*
 - switched broadcast, *1146*
 - digital, **1140ff**
 - broadcast, *1142*
 - cable, *1142*
 - recording, *1146*
- satellite, *1143*
 - spectrum, *1140s*
- display technology, *1146*
- HD, *1141*
- satellite
 - uplink, *1144p*
 - spectrum, *1141s*
 - tutorial, **1135ff**
- temperature
 - stabilized, *681*
 - oscillator, *450*
 - voltage reference, *676, 681*
- temperature coefficient
 - ways to specify, *683g*
- temperature controller, *see thermal controller*
- temperature sensor, *see sensor*
- termination
 - of transmission line, *739, 852ff, 1121*
- texting, *707n*
- Thévenin Equivalent Circuit, *69r*
- Thévenin equivalent circuit, **9ff, 69r**
 - examples, *1112*
- Thévenin's theorem, **1111ff**
 - generalized, *55*
- thermal controller, *123*
 - microcontroller, **1072–1080**
- thermal EMF, *see also op-amp, autozero, 339, 340, 675n*
- thermal hysteresis, *683*
- thermal resistance, *216, 603n, 624ff, 701r*
 - of heatsinks, *626g*
 - of PCB foil, *627g*
 - transient, *628, 702r, 1076*
- thermal runaway, *108ff, see asosecond breakdown108, 112, 187, 212ff, 214, 215*
 - absent in MOSFET, *138*
- thermistor, *see sensor*
- thermocouple, *see sensors, temperature*
- thyristor, *208, 581*
- TIA, *see transimpedance amplifier*
- time
 - delay
 - filter comparison, *404g*
 - delay circuit, *23*
 - hold, *see logic*
 - propagation, *see logic*
 - removal, *see logic*
- time constant, **22**
- timer, **457–469**, *470, 471r, 1100r*
 - 555, 460, 460*
 - an hour of power, *466*

- camera control (design example), 467
- ICs for, 468
- microcontroller as, 469
- one second per hour, 467
- programmable, 241
- timing
 - skew, 737n, 1030
- TinyLogic, *see* mini-logic
- tolerance, 6, 299, 388r
 - effect on filter response, 402g
- tools
 - favorites, 1156
- toroid, 581
 - common-mode choke, 584
- totem-pole, 697, 697
- touchscreen, 1085, 1087
- touchscreen digitizer, 946
- track-and-hold, *see also* op-amp, 256, 911
- tracking ADC, 911
- transconductance, *see also* BJT, FET, JFET, 89, 91
 - enhancer, 148
- transconductor, 99
- transducer, *see* sensor
- transfer function, 7
- transformer, **30**
 - bifilar winding, 656
 - for wideband ADC input, 382
 - gapped, 656, 670
 - in feedback loop, 286, 536
 - in switchmode converter, 653, 699r
 - inductance, *see* inductance
 - isolated SMPS, *see also* switchmode, **653ff**, **670**
 - isolation, 672
 - powerline, 632, 699r
 - leakage inductance in, 633
 - rating, 632
 - pulse
 - for isolated feedback, 663
 - signal, 497, **535–537**, 1128
 - signal isolator, 586
 - variable, 64p
- transient
 - averaging, *see* bandwidth, narrowing
 - capture, in PLL, 966
 - suppressor, 632, 670, 699r
 - thermal resistance, 628, 702r, 1076
- transient response
 - of voltage regulator, 617
- transimpedance amplifier, 233, 288r, 537, **537ff**, 547–549
- bandwidth, **537ff**
- bootstrapped cascode, 550, 550
- bootstrapping, 547
- capacitive feedback, 552, 571
- cascode input, **548ff**
- commercial, 570
- compensation, **539ff**, 540–542g
- composite, **543ff**, 544
 - noise, 544s
- current calibrator, 555
- JFET hybrid, **544**
- noise, 499, 511, 532, 593r
 - e_n -C, 540–542g, 542s, 543g
 - e_n C, 538, **538ff**
 - input, 538
 - reduction by bootstrapping, 547
- noise calculation, 539
- noise model, 539
- patch clamp, 552
- regulated cascode (RGC), 551
- stability, 537, 570
- STM, 553
- wideband
 - example, 540
 - world's best, 545
- transistor
 - bias-resistor, 712n, 827
 - bipolar, *see* BJT
 - BJT switch, 73–79, 91
 - diamond, 100
 - digital, 712n, 827
 - field-effect, *see* FET
 - man, 75
 - packages, 73p
 - pass, 594, 597, 598, 695, 699, 700r
 - protection, 695
 - perfect, 99
 - photo, **839**, 871p
 - power, **624ff**
 - pre-biased, 712n, 827
 - series connection of, 697
 - thermal resistance of, *see also* thermal resistance, 624
 - unijunction, 427, 428
- transistor)
 - switch, 127r
- transmission gate, *see* logic
- transmission line, **1120ff**
 - and sinewaves, **1124ff**
 - characteristic impedance, 1120

- derivation of, 1131
 - computer bus as, 1030
 - delay line, 1132p
 - differential, 880r
 - LVDS, **862–864**
 - rejection of common-mode signals, 860, 860s, 863, 863s
 - digital signals on, **852ff**, 880r
 - power dissipation, 868g
 - impedance matching, 1126
 - broadband lossless, 1128
 - minimum loss, 1127
 - narrowband lossless, 1129
 - reactive, 1129
 - transformer, 1128
 - loss, 1125, 1126g
 - matched
 - capacitance disappears, 1120
 - pre-emphasis, 858
 - reflection, 1030, 1121, 1122, 1123s
 - resistive attenuator, 1127, 1128t
 - ringing, 1123s
 - termination, **1121ff**
 - back, **1122**
 - series, **1122**
 - twisted pair, 1121
 - unterminated, 853, 854s, 1123
 - transresistance amplifier, *see* transimpedance amplifier
 - triac, 581, 691, 1065
 - quadrants, 692n
 - triangle wave, 15
 - triboelectric effect, 573
 - trigonometry, **1101**
 - truth table, *see* logic
 - TTL, *see* logic
 - TVS, 39, 670
 - twin-T filter, 414
 - twisted pair
 - wideband analog over, 352, 353
- UART, *see also* computer, **1041ff**, 1064, 1066, 1067, 1070, 1074, 1093, 1094, 1099
- bootloader, 1094
- ugly
 - diagram, 1106
- unblinking, 1003
- undersampling, *see also* ADC, *see* sampling
- undervoltage, 691
 - lockout, 701r
- unicast, 1146
- uninterruptible power supply (UPS), 673, 673s
- universe
 - age of, 771, 991
- unshielded twisted-pair, *see* UTP
- unused input, *see also* logic
- UPS, *see* uninterruptible power supply
- USB, *see also* computer, data bus, 1045, **1045**, 1065–1067, 1084, 1093, 1099r
 - bootloader, 1095
 - isolated, 1084
 - to RS-232 adapter, 865n, 1067
- UTP, 1121
- V to f*
 - conversion, *see* ADC
- varactor, *see also* diode, varactor, 64, 435, 962, 971, 973
 - tuned oscillator, 440, 470r
- Variac, 64p
- varistor, 39, 632
- VCO, *see* oscillator, voltage-controlled
- Verilog, *see also* logic, *see* programmable logic device (PLD), 711, 745, 765
- VGA, 1065, 1136n
- VHDL, *see* programmable logic device (PLD), 745, 765
- Victoreen, 3p, 698
- video
 - analog, 1136
 - coax, 1144
 - composite, 1137s
 - connectors, **1147ff**, 1148p
 - DAC, 1090
 - digitizer, 1088
 - encoder, 1033
 - field, 1137n
 - frame, 1136
 - interlaced, 1137n
 - modulation, 1137
 - multiplex, 1142
 - on demand, 1145
 - over Internet, 1144
 - progressive, 1137n
 - sync, 1137
- volt, 2
- voltage, **1**, 68r
 - as complex quantity, **44ff**
 - burden, 10
 - common-mode, *see* amplifier
 - comparator output swing, 810
 - compliance, 8
 - converter

- flying capacitor, 183
- divider, 7, 7
 - adjustable, 7
 - equation, 7
 - generalized, 48
- doubler, *see also* charge pump, 34, 34, 639, 660, 866, 1066
- drop
 - of diode, 31
- dropout, *see* voltage regulator, 599, 600, 700r
- Early, 93, 151n, 502
- electrostatic, 200t
- gain with RC , 71n
- high, *see* high voltage
- inverter, 639, 866, 1066
- Kirchhoff's voltage law, 2
- logic threshold, 796
- mode, *see* switchmode
- multiplier, 34
- noise, *see* noise
- offset, *see also* amplifier; op-amp, 366
 - cancelling V_{BE} , 85, 87
 - comparator, 812
 - correction with DAC, 951
 - JFET, 139, 512, 515
 - op-amp, 244
- offset in op-amp, *see* op-amp
- power-supply ripple, 33
- reference, *see* voltage reference, 700r
- regulator, *see* voltage regulator, 34
- signal, 14, 21–27
- source, 8
 - 8-channel, 895, 897
 - low-noise, 893, 894
 - stiff, 37
- source, general laboratory, 893, 894
- spike, *see* spike, *see* spike
- thermal, kT/Q , 136n
- thermal, kT/q , 91
- thermoelectric, 341t
- threshold
 - of digital logic, 797g
- triboelectric, 573
- voltage reference, 275, 674ff, 701r
 - 2-terminal, 677t
 - 3-terminal, 678t
 - accuracy, 683
 - bandgap, 104, 599, 602, 604 (box), 606, 611, 677, 678t, 679, 701r
 - as temperature sensor, 680
 - noise in, 679n
 - current source with, 898
 - drift, 683
 - humidity, 684
 - in DAQ, 951, 952
 - JFET pinchoff, 680, 680, 701r
 - line and load regulation, 684
 - low tempco, 676, 676, 681
 - MOSFET floating gate, 681, 701r, 914
 - noise, 682g, 682, 701r
 - precision, 681
 - PTAT, *see* PTAT
 - self-heating, 684
 - series, 674, 678t, 701r
 - shunt, 674, 677t
 - tempco, 683, 701r
 - ways to specify, 683g
 - temperature stabilized, 676, 681
 - trim, 683
 - V_{BE} , *see* voltage reference, bandgap
 - x-ray exposure, 684
 - zener, 674ff, 701r
 - biasing, 675
 - bootstrap biasing, 676
 - compared with bandgap, 679
 - compensated, 674
 - drift, 675
 - dynamic resistance, 675g
 - IC, 676ff, 677t
 - LTZ1000, the spectacular, 675
 - noise, 674, 676n
 - tempco, 675g
- voltage regulator, *see also* power supply, *see also* switchmode (SMPS), 82
 - 3-terminal, 700r
 - as current source, 620, 620, 621g
 - floating HV, 698
 - 317-style, 604 (box), 605t, 700r
 - adjustable to zero, 605, 607, 608
 - as current source, 620, 620, 621g
 - circuit, 606
 - dual voltage, 612
 - dual-tracking lab supply, 608
 - high-voltage supply, 609
 - hints, 604, 607
 - proportional fan control, 608
 - protection, 619
 - schematic, 603, 606
 - 337-style
 - schematic, 606

- 7800-style, 602t
- 723, **598ff**
 - in defense of, 600
- current limit, 693
 - foldback, 693
- current-reference, 611
- emitter follower as, 82
- extending V_{IN} , 211, 693
- fault protection, 619
- filtering, 619, 620
- floating, 698
- fully integrated, **600ff**
- high voltage, 609, 610, **695ff**, 696
- linear, 699r
 - 3-terminal adjustable, *see also* 317-style, **602ff**, 603
 - 3-terminal fixed, **601**, 602, 602t
 - adjustable to zero, 605, 607, 608, 611, 612
 - bypassing, 616
 - choosing, 613
 - crowbar, 598
 - current limit, 597
 - dropout voltage, 606g
 - error amplifier, 597
 - feedback stability, 597
 - ground-pin current, 616
 - high-voltage, 693, 698
 - idiosyncrasies, 613
 - LDO stability, 617, 617g
 - noise, 618
 - pinouts, 613
 - reverse polarity, 616
 - taxonomy, 601
 - transient response, 263g, 263s, 264, 617, 618s
 - tutorial, **595ff**, 596
- load dump, 618
- low-dropout, 561, 599, 700r
- low-dropout (LDO), 610, **610ff**, 611, 612g, 614, 615t
 - excess current near dropout, 616
 - stability, 617, 617g, 700r
- LT3080-style, 611, **611**
 - as current source, 620, 620, 621g
- op-amp, 235
- point-of-load (POL), 685
- protection, 606, 607, 619
- ramp-up control, 606n
- schematic, LM317, 603, 606
- schematic, LM337, 606
- switching, 609
 - taxonomy, 699r
 - zener as, 595
- voltmeter, 2
 - sensitive (design example), 253, 293
 - true rms, 568
- VOM, 10
- VSWR, 1125
- wall plug
 - blades and wires, 628n
- wall wart, 637n, 686
- wall-wart, 661
- watchdog, 755, 1062, 1064, 1067, 1070, 1082, 1100
- watt, 2
- wave
 - standing, 1125
- waveform
 - sampling, 419
- Wheeler's formula, 29
- wideband
 - analog link, 380
- Widlar, Bob, 97n, 101n, 102, 307, 598ff, 604 (box), 679
- Wien bridge, *see* oscillator
- WiFi, 1056, 1065
- Williams, Jim, 316n, 330, 438n, 1077, 1158
- Willison
 - John, 970
- Wilson mirror, *see also* current, mirror, 102, 102, 146
- window
 - averaging, 562n, 943g
 - discriminator, *see* AoE 2nd ed., p 669
 - quartz, 769, 1026
 - sampling, 420
 - tradeoffs, 421
 - switch, 573
- wire
 - in Verilog, 777
 - long
 - digital signals through, **850ff**, 879r, **1121**
- wired-AND, -OR, *see* logic
- wirewound resistor, *see* resistor, wirewound
- Words and Phrases, 714n
- world's best
 - DMM, 920
 - frequency-control algorithm, 1071
 - low e_n amplifier, 505
 - low distortion oscillator, 437
 - low-memory capacitor (Teflon), 301g
 - low-noise power supply, 578
 - multichannel fast $\Delta\Sigma$ ADC, 958

- op-amp noise plot, 526g, 531g
- precision current source, 900
- precision resistor, 227n, 300, 1110
- PWM DAC, 891
- TIA, 545
- voltage reference, 675, 677t, 681, 684, 894n, 922n
- worst-case specifications
 - violating, 296, 347, 388r
- write cycle, *see* memory; computer, programmed IO

- XOR, *see* logic, gates

- yesterday, 273 (box)

- ZCS, 1065
- zener, *see* diode, zener
 - active, 692, 692
- zero-crossing detector, 269
- zero-current switching, 650, 823
- zero-voltage switching, 650, 823
- ZigBee, 1056, 1064
- ZVS, 845, 1065
- ZVS, ZCS, *see also* switchmode